

**GOVERNMENT COLLEGE OF ENGINEERING, KALAHANDI**



**Lecture notes**

on

**BASIC ELECTRICAL ENGINEERING  
(Module I)**



**Associate Professor, Department of Electrical Engineering,  
Government College of Engineering, Kalahandi, Bhawanipatna, Odisha,  
India, PIN-766003.**

**Email: [debaprasad15@gmail.com](mailto:debaprasad15@gmail.com)**

## **Disclaimer**

This lecture note does not claim originality and is not intended to replace prescribed textbooks. It is a compilation prepared by the author(s) solely for educational purposes and to support teaching activities. Various sources, including those listed in the references section and publicly available material from the internet, have been consulted in its preparation. The ownership of the content lies with the respective authors or institutions. This lecture note is not intended for commercial use, and the author(s) are not liable for any issues, legal or otherwise, arising from its use. No guarantees are made regarding the accuracy or completeness of the content, and any implied warranties, including but not limited to merchantability or fitness for a particular purpose, are expressly disclaimed. The author(s) shall not be held responsible for any losses, including loss of profit or other damages, whether special, incidental, or consequential, that may result from the use of this document.

# **MODULE-I**

## **1. CIRCUIT ANALYSIS:**

### **1.1 Kirchhoff's Laws: -**

#### **1.1.1 Kirchhoff's current law or point law (KCL):**

**Statement:** - *In any electrical network, the algebraic sum of the currents meeting at a point is zero.*

$\Sigma I = 0$  .....at a junction or node

Assumption: - Incoming current = positive

Outgoing current = negative

#### **1.1.2. Kirchhoff's voltage law or mesh law (KVL):**

**Statement:** - *The algebraic sum of the products of currents and resistances in each of the conductors in any closed path (or mesh) in a network plus the algebraic sum of the emfs in that path is zero.*

$\Sigma IR + \Sigma emf = 0$  .....round the mesh

Assumption: - i) Rise in voltage (If we go from negative terminal to positive terminal) = positive

ii) Fall in voltage (If we go from positive terminal to negative terminal) = negative

iii) If we go through the resistor in the same direction as current then there is a fall in potential. Hence this voltage is taken as negative.


iv) If we go through the resistor against the direction of current then there is a rise in potential. Hence this voltage drop is taken as positive.

### **1.2. MAXWELL'S LOOP CURRENT METHOD (MESH ANALYSIS):**

**Statement:** - *This method determines branch currents and voltages across the elements of a network. The following process is followed in this method: -*

- Here, instead of taking branch currents (as in Kirchhoff's law) loop currents are taken which are assumed to flow in the clockwise direction.
- Branch currents can be found in terms of loop currents
- Sign conventions for the IR drops and battery emfs are the same as for Kirchhoff's law.

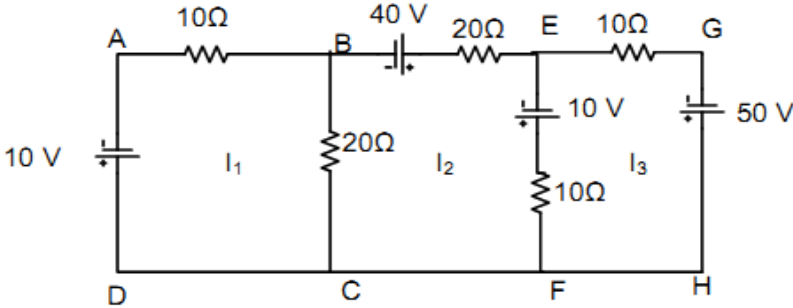**Example:** Find  $I_1$ ,  $I_2$  and  $I_3$  in the network shown in Fig below using loop current method.



$$\begin{aligned}
 -I_1 \times 10 - (I_1 - I_2) \times 20 - 10 &= 0 \\
 \Rightarrow 3I_1 - 2I_2 &= -1 \quad (1)
 \end{aligned}$$

For mesh BEFCB,

$$\begin{aligned}
 40 - I_2 \times 20 + 10 - (I_2 - I_3) \times 10 - (I_2 - I_1) \times 20 &= 0 \\
 \Rightarrow 2I_1 - 5I_2 + I_3 &= -5 \quad (2)
 \end{aligned}$$

For mesh EGHFE,

$$\begin{aligned}
 -10I_3 + 50 - (I_3 - I_2) \times 10 - 10 &= 0 \\
 \Rightarrow I_2 - 2I_3 &= -4 \quad (3)
 \end{aligned}$$

Equation (2) x 2 + Equation (3)

$$4I_1 - 9I_2 = -14 \quad (4)$$

Solving eq<sup>n</sup> (1) & eq<sup>n</sup> (4)

$$I_1 = 1 \text{ A}, I_2 = 2 \text{ A}, I_3 = 3 \text{ A}$$


### 1.3. NODAL ANALYSIS:

**Statement:** - This method determines branch currents in the circuit and also Voltages at individual nodes.

The following steps are adopted in this method: -

- Identify all the nodes in the network.
- One of these nodes is taken as reference node in at zero potential
- The node voltages are measured w.r.t the reference node
- KCL to find current expression for each node
- This method is easier if all the current sources are present. If any voltage source is present, convert it to current source.
- The number of simultaneous equations to be solved becomes (n-1) where 'n' is the number of independent nodes.

**Explanation: -**

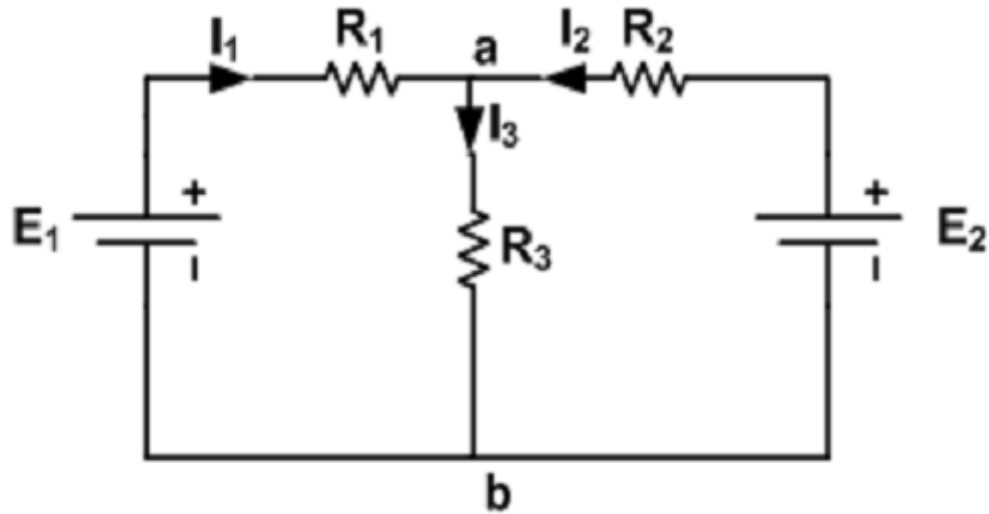

At node 'a'  $I_1 + I_2 = I_3$

By ohms law,  $I_1 = \frac{E_1 - V_a}{R_1}, I_2 = \frac{E_2 - V_a}{R_2}, I_3 = \frac{V_a}{R_3}$

Therefore,  $V_a \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{E_1}{R_1} - \frac{E_2}{R_2} = 0$


or,  $V_a \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{E_1}{R_1} - \frac{E_2}{R_2} = 0$

or,  $V_a \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{E_1}{R_1} - \frac{E_2}{R_2} = 0$


Hence,

- Node voltage multiplied by sum of the entire conductance connected to this node. This term is positive.
- The node voltage at the other end of each branch (connected to this node multiplied by conductance of this branch). This term is negative.

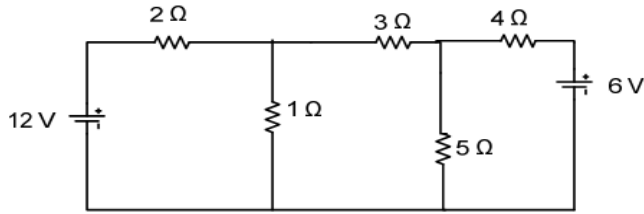**Example: -** Use nodal analysis to find currents in the different branches of the circuit shown below.



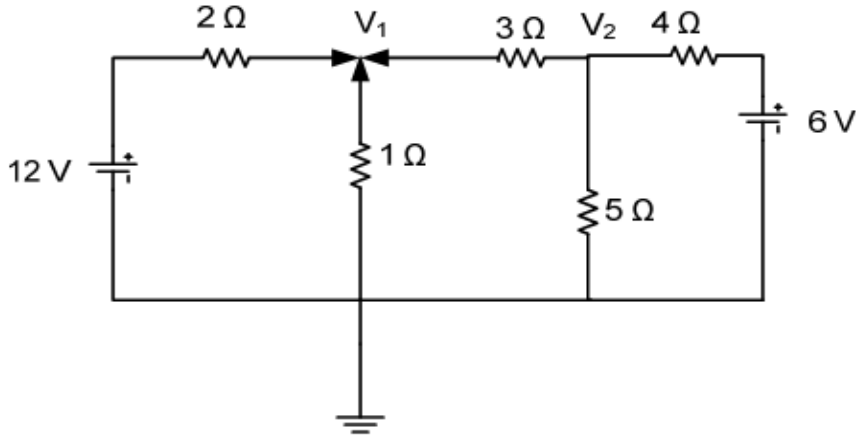**Solution:** - Let  $V_1$  and  $V_2$  are the voltages of two nodes as shown in Fig. below



Applying KCL to node-1, we get

$$\frac{12 - V_1}{2} + \frac{0 - V_1}{1} + \frac{V_2 - V_1}{3} = 0$$

$$\Rightarrow 36 - 3V_1 - 6V_1 + 2V_2 - 2V_1 = 0$$

$$\Rightarrow -11V_1 + 2V_2 = 36 \dots \dots \dots (1)$$

Again applying KCL to node-2, we get:-

$$\frac{V_1 - V_2}{3} + \frac{0 - V_2}{5} + \frac{6 - V_2}{4} = 0$$

$$\Rightarrow 20V_1 - 47V_2 + 90 = 0$$

$$\Rightarrow 20V_1 - 47V_2 = -90 \dots \dots \dots (2)$$

Solving Eq (1) and (2) we get  $V_1 = 3.924$  Volt and  $V_2 = 3.584$  volt

$$\text{Current through } 2 \Omega \text{ resistance} = \frac{12 - V_1}{2} = \frac{12 - 3.924}{2} = 4.038 \text{ A}$$

$$\text{Current through } 1 \Omega \text{ resistance} = \frac{0 - V_1}{1} = -3.924 \text{ A}$$

$$\text{Current through } 3 \Omega \text{ resistance} = \frac{V_1 - V_2}{3} = 0.1133 \text{ A}$$

$$\text{Current through } 5 \Omega \text{ resistance} = \frac{0 - V_2}{5} = -0.7168 \text{ A}$$

$$\text{Current through } 4 \Omega \text{ resistance} = \frac{6 - V_2}{4} = 0.604 \text{ A}$$

As currents through  $1\Omega$  and  $5\Omega$  are negative, so actually their directions are opposite to the assumptions.

## Series Circuit Resistors:

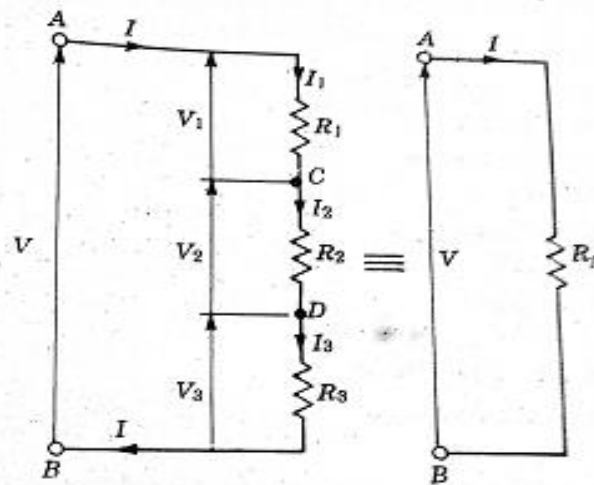


Fig. 4.13. Series circuit and its equivalent.

By KVL in mesh A - C - D - B - A

$$V_{AC} + V_{CD} + V_{DB} + V_{BA} = 0 ; -V_1 - V_2 - V_3 + V = 0$$
$$V = V_1 + V_2 + V_3$$

By Ohm's law

$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$V_3 = R_3 I$$

From the equivalent circuit shown in Fig. 4.13 (b),

$$V = R_S I$$

Combining the Eqs. (4.7.1) to (4.7.5) we get

$$R_S I = R_1 I + R_2 I + R_3 I$$

$$R_S = R_1 + R_2 + R_3$$

## Parallel Ckt. Resistors:

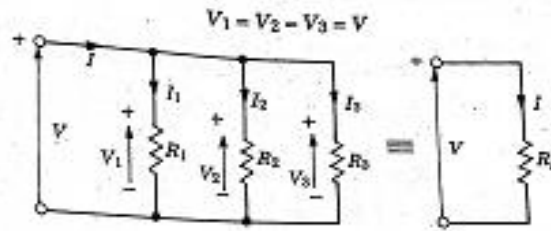


Fig. 4.17. Resistors in parallel and their equivalent.

We are interested in finding a single resistance  $R_p$  which has the same volt-ampere relation combination.

By KCL,

$$I = I_1 + I_2 + I_3$$

By Ohm's law

$$I_1 = \frac{V_1}{R_1} = \frac{V}{R_1}$$

$$I_2 = \frac{V_2}{R_2} = \frac{V}{R_2}$$

$$I_3 = \frac{V_3}{R_3} = \frac{V}{R_3}$$


$$I = \frac{V}{R_p}$$

Substituting these values in Eq. (4.11.1)

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

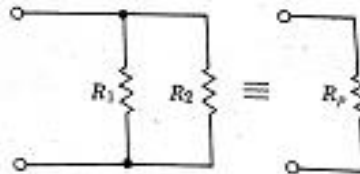When only two resistors are in parallel (Fig. 4.18)




$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$


$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{\text{product}}{\text{sum}}$$

No

Step-I

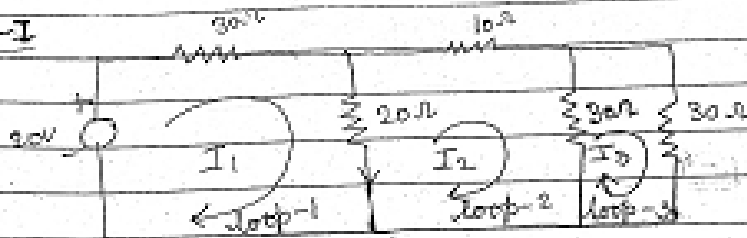

Step-2 (Consider loop-1 and apply KVL)

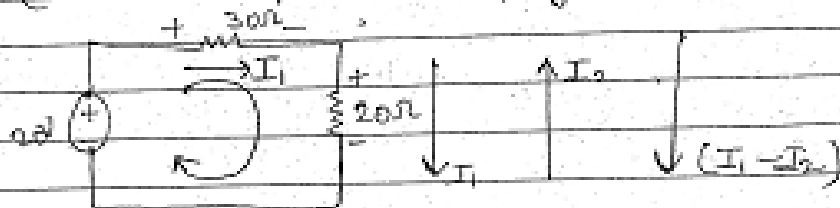


$$20 - 30I_1 - 20(I_1 - I_2) = 0$$

$$\Rightarrow 20 - 30I_1 - 20I_1 + 20I_2 = 0$$

$$\Rightarrow 50I_1 - 20I_2 = 20$$

$$\Rightarrow 50I_1 - 20I_2 + 0I_3 = 20 \quad \text{--- (1)}$$

Step-3 (Consider loop-2 and apply KVL)

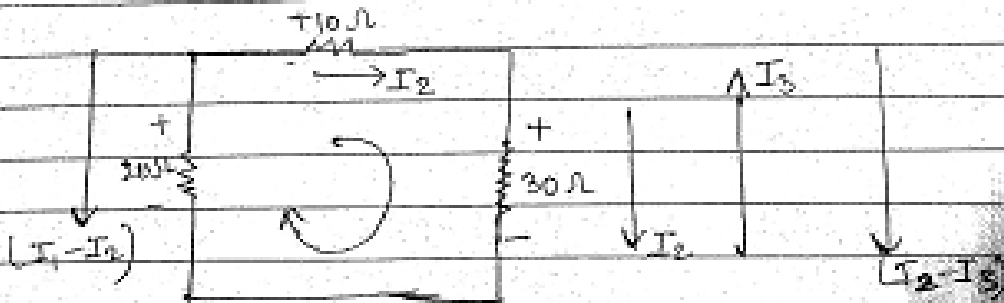

Solve the above ckt. By using KVL. And also Loop analysis method (mesh)

$$20(I_1 - I_2) - 10I_2 - 30(I_2 - I_3) = 0$$

$$\Rightarrow 20I_1 - 20I_2 - 10I_2 - 30I_2 + 30I_3 = 0$$

$$\Rightarrow 20I_1 - 60I_2 + 30I_3 = 0 \quad \text{--- (2)}$$

Step-4 (Considered loop-3 and apply kvl)



$$30(I_2 - I_3) - 30I_3 = 0$$

$$\Rightarrow 30I_2 - 60I_3 = 0$$

$$\Rightarrow 0I_1 + 30I_2 - 60I_3 = 0$$

from eq (1), (2) & (3) can be written in matrix form

$$50I_1 - 10I_2 + 0I_3 = 20 \quad \text{--- (1)}$$

$$20I_1 - 60I_2 + 30I_3 = 0 \quad \text{--- (2)}$$

$$0I_1 + 30I_2 - 60I_3 = 0 \quad \text{--- (3)}$$

50	-10	0	$I_1$	=	20
20	-60	30	$I_2$	=	0
0	30	-60	$I_3$	=	0

$$\Delta = \begin{vmatrix} 50 & -20 & 0 \\ 20 & -60 & 30 \\ 0 & 30 & -60 \end{vmatrix} = 111000$$

$$\Delta_1 = \begin{vmatrix} 20 & -20 & 0 \\ 0 & -60 & 30 \\ 0 & 30 & -60 \end{vmatrix} = 54000$$

$$\Delta_2 = \begin{vmatrix} 50 & 20 & 0 \\ 20 & 0 & 30 \\ 0 & 0 & -60 \end{vmatrix} = 24000$$


$$\Delta_3 = \begin{vmatrix} 50 & -20 & 20 \\ 20 & -60 & 0 \\ 0 & 30 & 0 \end{vmatrix} = 12000$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{54000}{111000} = 0.49 \text{ Amp}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{24000}{111000} = 0.22 \text{ Amp}$$


$$I_3 = 0.11 \text{ Amp}$$

10/1/18

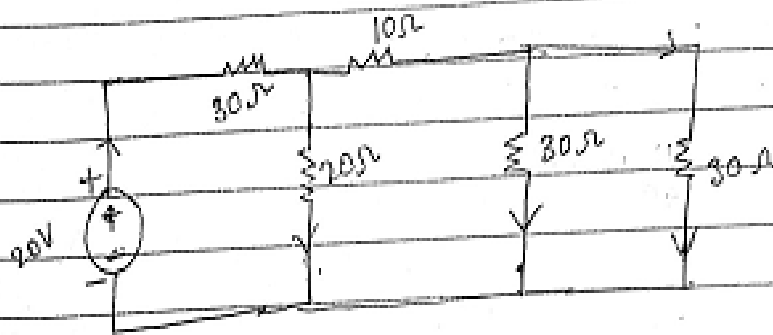

Find current, voltage and power in 20Ω Resistor using nodal analysis

Step-1

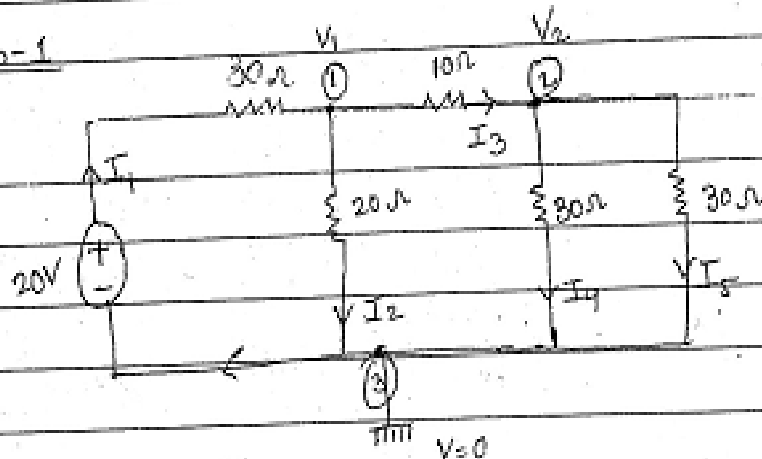

Junctions  $\rightarrow$  3

voltage of earthing = 0

When source gives current it is positive when it receives it is negative

Step-2, (Consider junction-1 and apply KCL)

$$I_1 = I_2 + I_3$$

$$I_1 \Rightarrow \frac{0 + 20 - V_1}{30} = \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{10}$$

$$\Rightarrow \frac{20}{30} - \frac{V_1}{30} = \frac{V_1}{20} + \frac{V_1}{10} - \frac{V_2}{10}$$

$$\Rightarrow V_1 \left( \frac{1}{30} + \frac{1}{20} + \frac{1}{10} \right) - \frac{V_2}{10} = \frac{2}{3}$$

$$\Rightarrow V_1 \left( \frac{2+3+6}{60} \right) - \frac{V_2}{10} = \frac{2}{3}$$

$$\Rightarrow \frac{11}{60} V_1 - \frac{V_2}{10} = \frac{2}{3}$$

$$\Rightarrow 11V_1 - 6V_2 = 40 \quad (1)$$

Step-2:- (Consider junction-2 and apply KCL)

$$I_3 = I_4 + I_5$$

$$\Rightarrow \frac{V_1 - V_2}{10} = \frac{V_2 - 0}{30} + \frac{V_1 - 0}{30}$$

$$\Rightarrow \frac{V_1}{10} - \frac{V_2}{10} = \frac{V_2}{30} + \frac{V_1}{30}$$

$$\Rightarrow \frac{V_1 - V_2}{10} = \frac{2V_2}{30}$$

$$\Rightarrow \frac{V_1 - V_2}{10} = \frac{V_2}{15}$$

$$\frac{3}{15} (V_1 - V_2) = \frac{2}{15} V_2$$

$$3V_1 - 3V_2 = 2V_2$$

$$3V_1 - 3V_2 - 2V_2 = 0$$

$$3V_1 - 5V_2 = 0 \quad \text{--- (2)}$$

from (1) & (2)

$$11V_1 - 6V_2 = 40 \quad \times 3$$

$$3V_1 - 5V_2 = 0 \quad \times 11$$

$$33V_1 - 18V_2 = 120$$

$$33V_1 - 55V_2 = 0$$

$$\begin{array}{r} (-) \quad (+) \quad (-) \\ \hline \end{array}$$

$$37V_2 = 120$$

$$V_2 = \frac{120}{37} = 3.24 \text{ volt}$$

$$V_1 = 5.41 \text{ volt}$$

$$\text{So } I_2 = \frac{V_1 - 0}{20} = \frac{5.41}{20} = \underline{\underline{0.27 \text{ Amp.}}}$$

$$V_{20} = I_2 \times 20 = 0.27 \times 20 = 5.41 \text{ volt}$$


$$P_{20} = V_{20} \times I_2 = 5.41 \times 0.27 = 1.46 \text{ watt}$$

## Current - divides Equations : →

Let us two resistances  $R_1$  &  $R_2$  are connected in parallel.

Again  $R_p$  = total resistance of the parallel ckt.

$I$  = total current of the ckt.

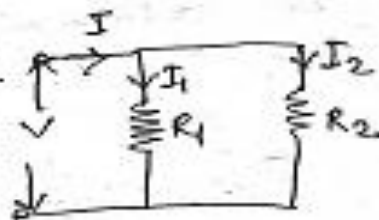

$$R_p = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \text{Total resistance of the ckt.}$$

$$I = \frac{V}{R_p} \quad \text{Similarly } I_1 = \frac{V}{R_1} \quad \& \quad I_2 = \frac{V}{R_2}$$

$$\frac{I_1}{I} = \frac{V/R_1}{V/R_p} = \frac{R_p}{R_1} = \frac{1}{R_1} \cdot \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\frac{I_1}{I} = \frac{R_2}{R_1 + R_2} \Rightarrow \boxed{I_1 = \frac{R_2 I}{R_1 + R_2}}$$


For  $I_2$

$$\frac{I_2}{I} = \frac{V/R_2}{V/R_p} = \frac{R_p}{R_2} = \frac{1}{R_2} \cdot \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\boxed{I_2 = \frac{R_1 I}{R_1 + R_2}}$$

- \* Three resistances of values  $4\ \Omega$ ,  $6\ \Omega$  and  $8\ \Omega$  are connected in series across a  $36\text{V}$  dc supply. Calculate (a) total resistance of the ckt. (b) total current of the ckt. (c) voltage drop across each resistance (d) power dissipated in each resistance (e) total power dissipated in the ckt.

Soln:

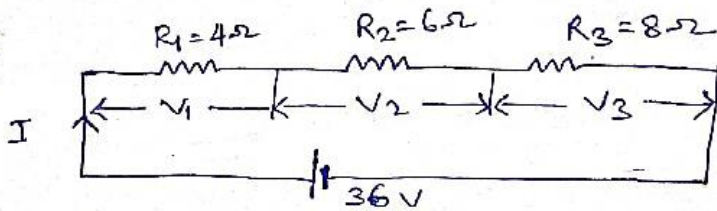

- (a) total resistance ( $R_s$ ) =  $R_1 + R_2 + R_3 = 4 + 6 + 8 = 18\ \Omega$
- (b) total current of the ckt.  $I = \frac{V}{R_s} = \frac{36}{18}$   
 $I = 2\text{ Amp.}$

- (c) Voltage drop across  $4\ \Omega$  resistor

$$V_1 = R_1 I = 4 \times 2 = 8\text{V}$$

voltage drop across  $6\ \Omega$  resistor

$$V_2 = R_2 I = 6 \times 2 = 12\text{V}$$

voltage drop across  $8\ \Omega$  resistor

$$V_3 = R_3 I = 8 \times 2 = 16\text{V}$$

$$\text{Total voltage } V_s = V_1 + V_2 + V_3 = 8 + 12 + 16 = 36\text{V}$$

- (d) Power dissipated in  $4\ \Omega$  resistance

$$P_1 = I^2 R_1 = (2)^2 \times 4 = 16\text{W}$$

power dissipated in  $6\ \Omega$  resistance

$$P_2 = I^2 R_2 = (2)^2 \times 6 = 24\text{W}$$

power dissipated in  $8\ \Omega$  resistance is

$$P_3 = I^2 R_3 = (2)^2 \times 8 = 32\text{W}$$


- (e) Total power dissipated in ckt. is

$$P = P_1 + P_2 + P_3 = 16 + 24 + 32 = 72\text{W}$$

$$P = 72\text{ watt}$$

OR

$$P = VI = 36 \times 2 = 72\text{W}$$

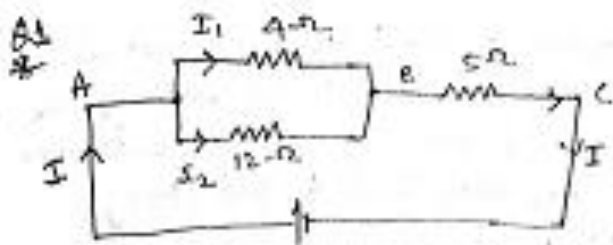

For this network determine

(a) voltage drop in each resistor

(b) Current in each resistor.

Sol<sup>n</sup> Ist Calculate the total resistance of parallel ckt. A||B

$$\frac{1}{R_{AB}} = \frac{1}{4} + \frac{1}{12} = \frac{1}{3} \left[ R_{AB} = \frac{4 \times 12}{4+12} = \frac{48}{16} = 3 \Omega \right]$$

$$R_{AB} = 3 \Omega, V_{AC} = I \times R_{AC} = 10 \times 8 = 80 \text{ V}$$

$$R_{AC} = R_{AB} + R_{BC} = 3 + 5 \Rightarrow R_{AC} = 8 \Omega$$

voltage drop across 5-ohm resistor

$$V_{BC} = R_{BC} I = 5 \times 10 \Rightarrow V_{BC} = 50 \text{ V}$$

$$V_{AC} = V_{AB} + V_{BC}$$

$$\Rightarrow 80 = V_{AB} + 50 \Rightarrow V_{AB} = 30 \text{ V}$$


voltage drop across 4-ohm resistor

= voltage drop across 12-ohm resistor = 30 V.

$$I_1 = \frac{V_{AB}}{4} = \frac{30}{4} \Rightarrow I_1 = 7.5 \text{ A}$$

$$I_2 = \frac{V_{AB}}{12} = \frac{30}{12} \Rightarrow I_2 = 2.5 \text{ A}$$

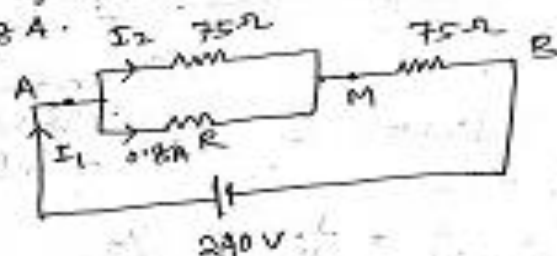Q.2 A  $150\Omega$  resistance coil AB is connected across  $240V$  dc supply. Calculate the value of the resistance which, when connected between the midpoint of AB and end A, will carry a current of  $0.8A$ .



Sol<sup>n</sup>

Let  $M$  be the mid point of  $AB$  and  $R$  be the resistance between  $A$  and  $M$  and let  $I_R = 0.8A$

$$\text{voltage across } R_{MB} = R_{MB} I_1 = 75 I_1$$

$$V_{AB} = V_{AM} + V_{MB} \Rightarrow V_{AM} = V_{AB} - V_{MB}$$

$$V_{AM} = 240 - 75 I_1$$

By KCL at point  $A$ .

$$I_1 = I_2 + 0.8 \Rightarrow I_1 = \frac{V_{AM}}{75} + 0.8$$

$$I_1 = \frac{240 - 75 I_1}{75} + 0.8$$

$$\Rightarrow 75 I_1 = 240 - 75 I_1 + 0.8 \Rightarrow I_1 = \frac{310}{150}$$

$$\boxed{I_1 = 2A}$$

$$V_{AM} = 240 - 75 \times 2 \Rightarrow \boxed{V_{AM} = 90V}$$

$$R = \frac{V_{AM}}{0.8} \Rightarrow R = \frac{90}{0.8} \Rightarrow \boxed{R = 112.5\Omega}$$

Q.3. A DC ckt. comprises two resistors, A of value  $25\ \Omega$ , and B of unknown value, connected in parallel together with a third resistor C of the value  $5\ \Omega$  connected in series with the parallel group. The potential difference across C is  $90\ \text{V}$ . If the total power in the ckt. is  $4320\ \text{W}$ , Calculate -


- The value of resistor B.
- The voltage applied to the ends of the whole ckt.
- The current in each resistor.

Sol<sup>n</sup>

For this ckt.

$$\textcircled{a} \quad I = \frac{90}{5} = 18\ \text{A}$$

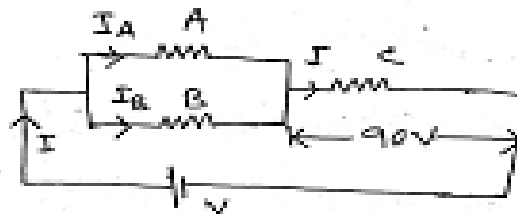If  $R_p$  is the total resistance of the ckt. then



total power will be

$$P = I^2 R_p \Rightarrow 4320 = I^2 R_p$$

$$R_p = \frac{4320}{(18)^2} \Rightarrow R_p = 40/3\ \Omega$$

But  $R_p = \frac{25B}{B+25} + 5$

so

$$\frac{25B}{B+25} + 5 = 40/3 \Rightarrow \boxed{B = 12.5\ \Omega}$$

$\textcircled{b}$  voltage applied to the end of whole

$$\text{ckt.} \Rightarrow V = R I = \frac{40}{3} \times 18 = 240\ \text{V}$$

$$\boxed{V = 240\ \text{V}}$$

© Current in each resistor.

Current in resistor C =  $I = 18 \text{ A}$ .

But the total voltage across the whole ckt. =  $240 \text{ V}$ .

So the voltage across the parallel branch = Total voltage across whole ckt. - voltage across resistor C.

$$\Rightarrow 240 - 90 = 150 \text{ V.}$$

voltage across parallel branch =  $150 \text{ V}$ .

Current in resistor A is

$$\Rightarrow I_A = 150/25$$


$$I_A = 6 \text{ A}$$

Current in resistor B is

$$\Rightarrow I_B = 150/12.5$$


$$I_B = 12 \text{ A}$$

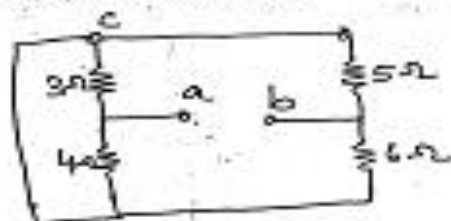Q.4 Determine the resistance between the terminals a-b in the network.



Soln

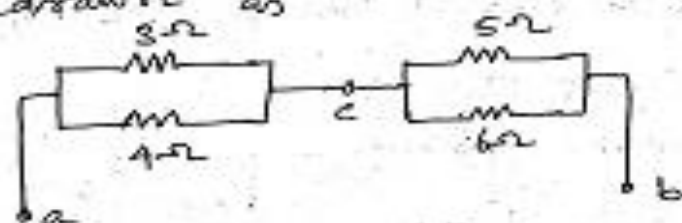The network of fig above fig. can be redrawn as



$$R_{ac} = \frac{3 \times 4}{3 + 4} = \frac{12}{7} \Omega$$

$$R_{bc} = \frac{5 \times 6}{5 + 6} = \frac{30}{11} \Omega$$

$$R_{ab} = R_{ac} + R_{bc} = \frac{12}{7} + \frac{30}{11}$$

$$R_{ab} = 4.44 \Omega$$

## NETWORK THEOREMS:

SUPERPOSITION THEOREM

THEVENIN'S THEOREM


NORTON'S THEOREM

MAXIMUM POWER TRANSFER


### SUPERPOSITION THEOREM:

**Statement:** - In a network of linear resistances containing more than one generator (or source of) of all the currents which would flow at that point if each generator were considered separately and all the other generators replaced for the time being by resistances equal to their internal resistance.

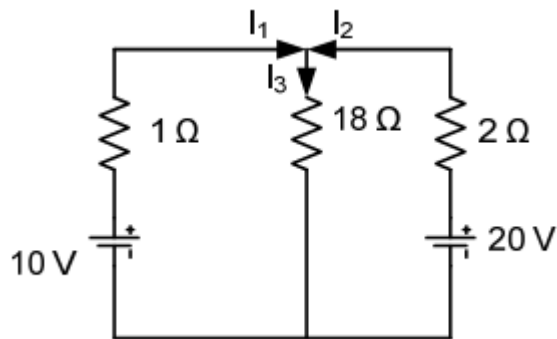Example: - By using superposition theorem, calculate the currents in the network shown.



Step 1. Considering 10 V battery

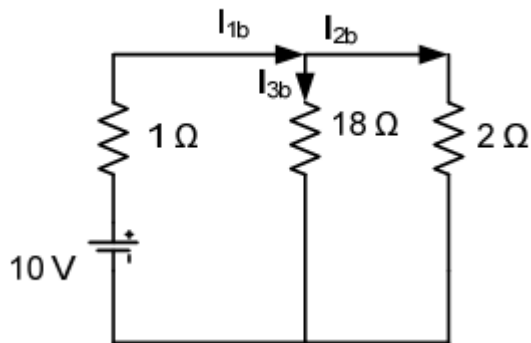


$$R_{eq} = \frac{2 \times 18}{2 + 18} + 1 = 2.8 \Omega$$

$$I_{1b} = \frac{10}{2.8} = 3.57 \text{ A}$$

$$I_{2b} = 3.57 \times \frac{18}{20} = 3.21 \text{ A}$$

$$I_{3b} = I_{1b} - I_{2b} = 0.36 \text{ A}$$

Step 2. Considering 20 V battery

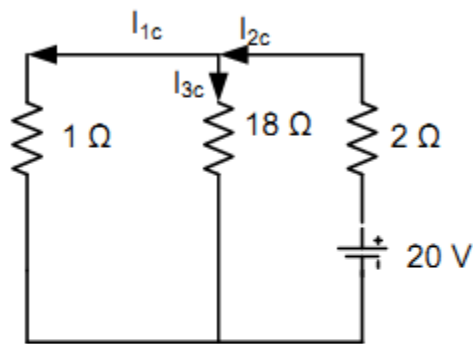

$$R_{eq} = \frac{1 \times 18}{1 + 18} + 2 = 2.95 \Omega$$

$$I_{2c} = \frac{20}{2.95} = 6.78 \text{ A}$$

$$I_{1c} = 6.78 \times \frac{18}{19} = 6.42 \text{ A}$$

$$I_{3b} = I_{2c} - I_{1c} = 0.36 \text{ A}$$

Step 3. Results

$$I_1 = I_{1b} - I_{1c} = 3.57 - 6.42 = -2.85 \text{ A}$$


$$I_2 = I_{2c} - I_{2b} = 6.78 - 3.21 = 3.57 \text{ A}$$

$$I_3 = I_{3b} + I_{3c} = 0.36 + 0.36 = 0.72 \text{ A}$$

### SOURCE CONVERSION: -

Statement: A voltage source ( $V$ ) with a series resistance ( $R$ ) can be converted to a current source ( $I=V/R$ ) with a parallel resistance ( $R$ ) and vice-versa.

Explanation:

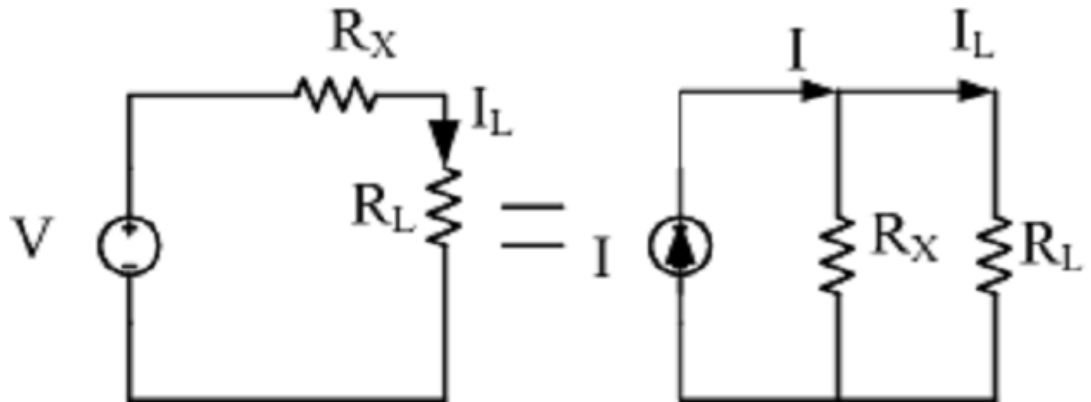

$$I_L = \frac{V}{R_X + R_L} \quad (1)$$

$$I_L = I \frac{R_X}{R_X + R_L} \quad (2)$$


From Eq. (1) & (2)

$$V = IR_X \quad (3)$$

### Summary:

- The two circuits are said to be electrically equivalent if they supply equal load currents with the same resistance connected across their terminals.
- Voltage source having a voltage  $V$  and source resistance  $R_x$  can be replaced by  $I(= V/R_x)$  and a source resistance  $R_x$  in parallel with current source.
- Current source  $I$  and source resistance  $R_x$  can be replaced by a voltage source  $V (=IR_x)$  and a source resistance  $R_x$  in series with  $V$ .

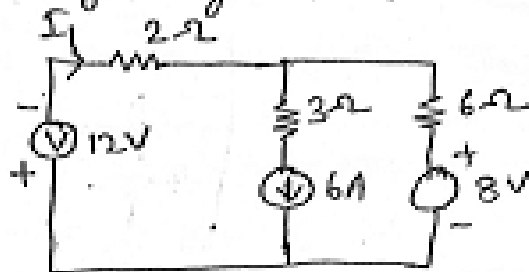
Q.5 Determine the branch current  $I_1$  in the given ckt. by using Superposition theorem.



Sol<sup>n</sup> There are three sources in the above ckt. we have to calculate current through  $2\Omega$  resistor.

Step-1 Consider only 12V source -

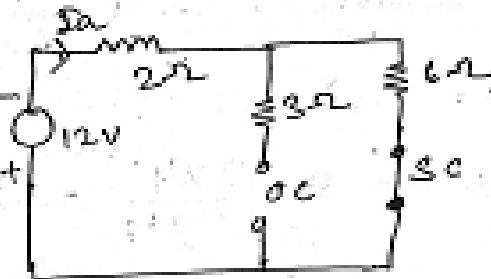The 6A current source is open-circuited & the 8V voltage is short ckt. The resulting ckt. is




given in this fig. There is no current through open ckt. Hence the current through  $3\Omega$  resistor is zero. By ohm's law

$$I_a = \frac{-12}{2+6} = -1.5 \text{ Amp.}$$

Step-2 : Consider only 6Amp current in the ckt

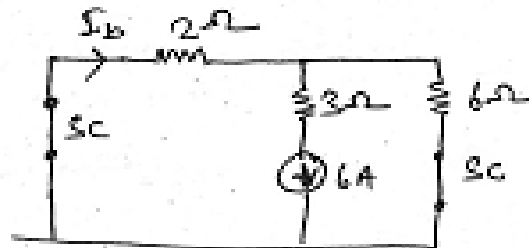The 12V voltage source and 8V voltage source is short circuited.



... is a current through open ckt. Hence


The 6A current source is supplying current to  $2\Omega$  and  $6\Omega$  resistors in parallel.

By current division rule

$$I_b = \frac{6}{2+6} \times 6 = 4.5 \text{ A.}$$

© Consider only 8V source in the ckt.

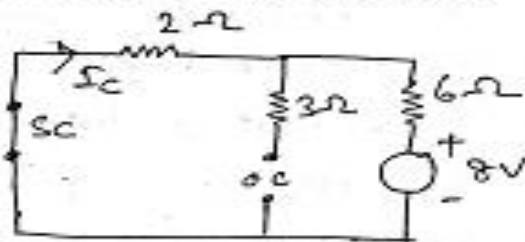The 6Amp current source is open ckt. and 12V voltage source is short ckted.



By Ohm's Law -

$$I_c = \frac{-8}{6+2} = -1 \text{ A.}$$

By superposition principle, the total current through the  $2\Omega$  resistor is  $\Rightarrow I_1 = I_a + I_b + I_c$


$$I_1 = -1.5 + 4.5 - 1$$

$$I_1 = 2 \text{ amp}$$


## THEVENIN'S THEOREM: -

**Statement:-** Any pair of terminals  $AB$  of a linear active network may be replaced by an equivalent voltage source in series with an equivalent resistance  $R_{th}$ . The value of  $V_{th}$  (called the Thevenin's voltage) is equal to potential difference between the terminals  $AB$  when they are open circuited, and  $R_{th}$  is the equivalent resistance looking into the network at  $AB$  with the independent active sources set to zero i.e with all the independent voltage sources short-circuited and all the independent current sources open-circuited.

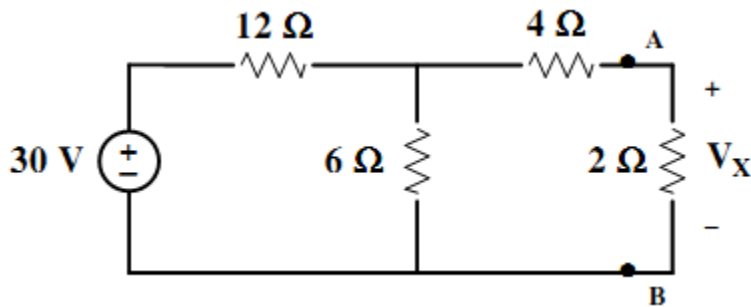Example: - Find  $V_X$  by first finding  $V_{TH}$  and  $R_{TH}$  to the left of A-B.



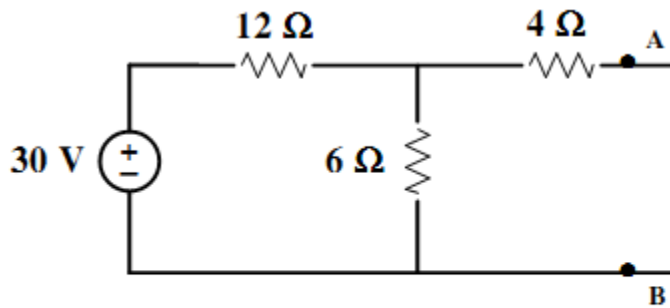
Solution: step1. First remove everything to the right of A-B



$$V_{AB} = \frac{(30)(6)}{6 + 12} = 10V$$


There is no current flowing in the 4Ω resistor (A-B) is open. Thus, there can be no voltage across the resistor.

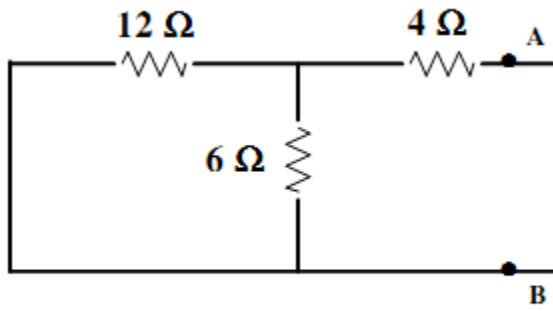Step 2. To find  $R_{th}$ : We now deactivate the sources to the left of A-B and find the resistance seen looking in these terminals.



$$R_{TH} = 12 \parallel 6 + 4 = 8 \Omega$$

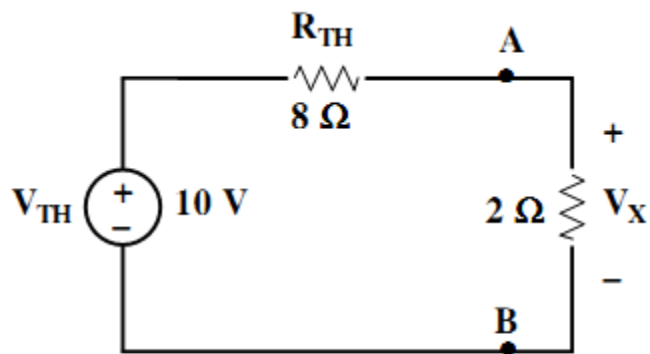Step 3. To find  $V_x$  : After having found the Thevenin circuit, we connect this to the load in order to find  $V_x$ .




$$V_x = \frac{(10)(2)}{2+8} = 2V$$

Q.6 Determine the current through and voltage across the  $25\Omega$  resistor by using Thevenin's law.

Soln

Step 1  $\rightarrow$  First

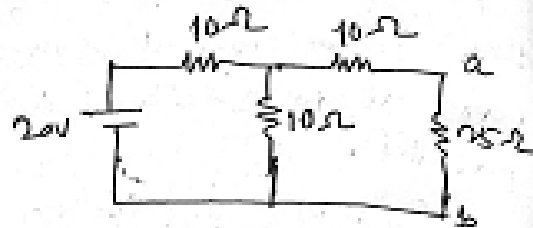disconnect the  $25\Omega$  resistor from the original network.



Step 2  $\rightarrow$  Determination of  $V_{th}$

Since, the ckt is open between a-b, there is no current will flow in  $R_2$ . So that


there is no voltage drop in  $R_2$

so the  $V_{ab}$  = voltage drop

across  $R_3 = R_3 I_1$

$$\Rightarrow R_3 \frac{V_s}{R_1 + R_3}$$

$$= 10 \times \frac{20}{10 + 10} = 10V$$

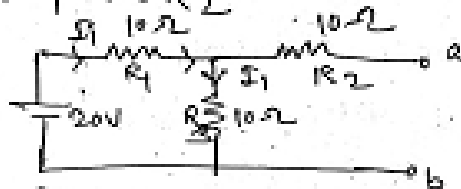


$$V_{R_2} = 10V$$

$$\text{So } V_{th} = \text{oc voltage} = 10V$$

Step 3 The voltage across


the 20V source is shorted.

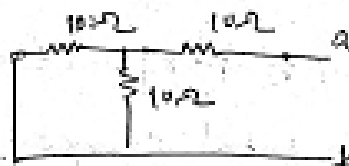

$$R_{th} = R_2 + \frac{R_1 \times R_2}{R_1 + R_2} = 15\Omega$$


$$R_{th} = 15\Omega$$

Step-4

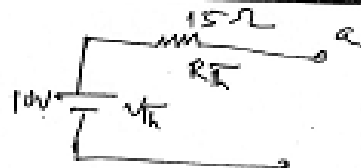

Current through  $25\Omega$  resistor is to be calculated

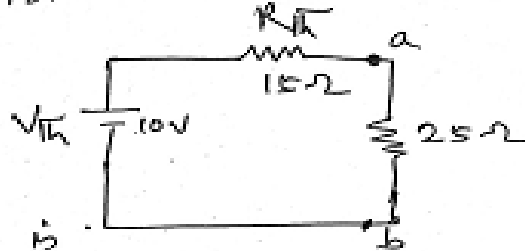The  $25\Omega$  resistor is connected between a-b



Let  $I$  be the total current flowing across  $25\Omega$  resistor.

$$I = \frac{V_{th}}{R_{th} + R_s} = \frac{10}{15 + 25}$$


$$I = 0.25 \text{ Amp}$$

Voltage across  $25\Omega$  resistor is


$$= 25 I = 25 \times 0.25 \text{ resistor}$$

$$= \cancel{0.25} \text{ } \boxed{6.25 \text{ Amp}}$$

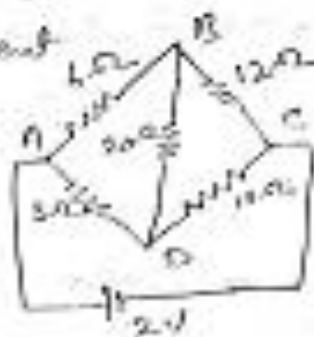Q.7 Determine the current in  $20\ \Omega$  resistor by using Thevenin's theorem.



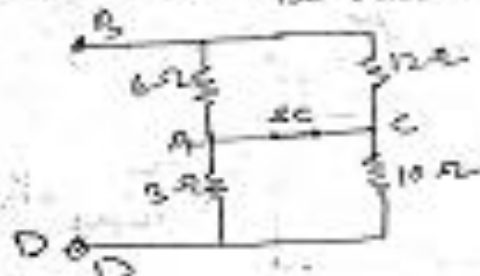Soln Step I :- The fig. can be redrawn as



calculate  $V_{th}$  :- ~~Imagine the resistor~~

Let the resistor between B and D is removed  
 so current through ABC  $\Rightarrow I_{AC} = \frac{2}{6+12} = \frac{1}{9}\text{ A}$

voltage across AB  $R_{AB}$  is  $V_{AB}$

$$V_{AB} = R_{AB} I_{AC} = 6 \times \frac{1}{9} = \frac{2}{3}\text{ V}$$

$$I = \frac{V}{R}$$

Current through ADC =  $\frac{2}{3+10} = \frac{2}{13}\text{ A}$

$$I_{AD} = \frac{2}{13}\text{ A}$$

voltage drop across AD is  $V_{AD}$

$$= R_{AD} I_{AD} = 3 \times \frac{2}{13} = \frac{6}{13}\text{ A}$$

apply mesh ABDA by KVL

$$V_{AB} + V_{BD} + V_{DA} = 0$$

$$V_{BD} = -V_{DA} - V_{AB} \Rightarrow V_{BD} = -V_{AD} - V_{AB}$$

$$V_{BD} = \frac{6}{13} - \frac{2}{3} = -\frac{8}{39}\text{ V}$$


$$V_{BD} = -\frac{8}{29} \text{ V}$$

$$V_{DB} = \frac{8}{29} \text{ V}$$

$$V_{Th} = V_{DB} = \frac{8}{29} \text{ V}$$

Calculate  $R_{Th}$

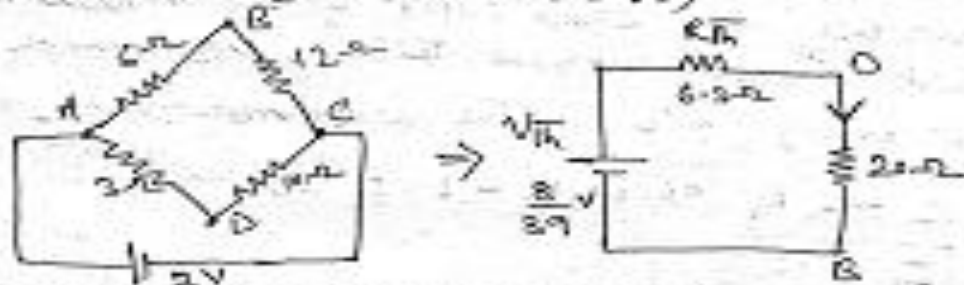$R_{Th}$  is the resistance between terminal B and D with  $20\Omega$  resistor removed and replacing the battery with its internal resistance (zero in this case).



Total resistance through AD =  $R_{AD} = R_{AB} \parallel R_{BC} + R_{CD} \parallel R_{DA}$

$$R_{AD} = (R_{AB} \parallel R_{BC}) + (R_{CD} \parallel R_{DA})$$

$$= \frac{6 \times 12}{6 + 12} + \frac{3 \times 10}{3 + 10} = 6.3 \Omega$$

$$R_{Th} = R_{AD} = 6.3 \Omega$$


Current through  $20\Omega$  resistor =  $I_{20} = \frac{V_{Th}}{R_{Th} + R_{20}}$

$$I_{20} = \frac{8/29}{6.3 + 20} = 7.8 \text{ mA from D to B}$$

$$I_{20} = 7.8 \text{ mA}$$

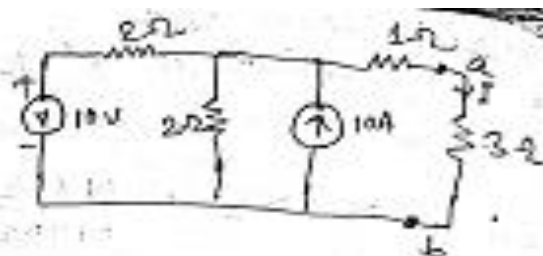
Q.9

Determine the current  $I$  in the network by using Thevenin's theorem.




Soln Step-1 - Now the  $3\Omega$  resistor through which  $I$  is flowing is removed

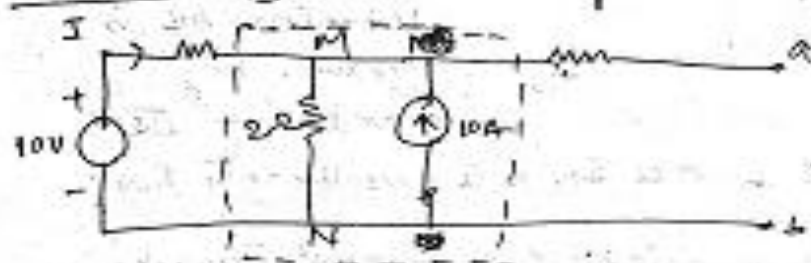Step-2 Determination of Thevenin voltage  $V_{th}$



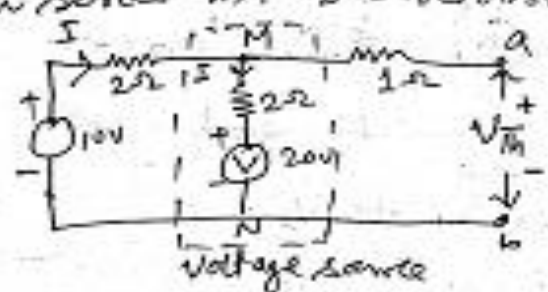The  $10A$  current is parallel with  $2\Omega$  resistor is transformed to a  $10 \times 2 = 20V$  source in series with  $2\Omega$  resistor



Here the current through  $1\Omega$  resistor is zero because of the open ckt. between terminal  $a-b$ .

Now apply KVL to the left hand side

$$10 - 2I - 2I - 20 = 0$$

$$I = -10/4 = -2.5 A.$$

$$I = 2.5 A$$

AP Apply KVL to right hand side

$$20 + 2I - V_{Th} = 0$$


$$V_{Th} = 20 + 2I = 20 + 2 \times (2.5)$$

$$V_{Th} = 15V$$

Step-3 Determination of Thevenin resistance

$R_{Th}$

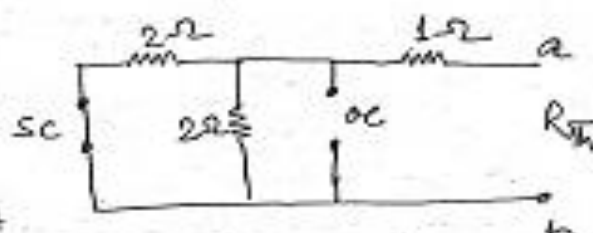
The 10V voltage source is short ckted and the 10A current source is open ckted. Now Thevenin resistance  $R_{Th}$  is = resistance between the terminal a-b



Thevenin resistance  $R_{Th}$  is = resistance between the terminal a-b

$$= 1 + 2 \parallel 2 = 1 + \frac{2 \times 2}{2+2} = 2 \Omega$$

Step-4 Thevenin equivalent network

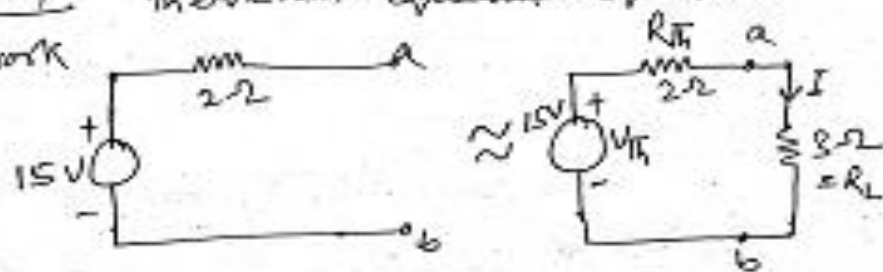

Step-5 Determination of current through 3Ω resistor is  $\Rightarrow I = \frac{V_{Th}}{R_{Th} + R_L} = \frac{15}{2+3}$

$$I = 3A$$

## NORTON'S THEOREM:

**Statement:** Any two terminal linear active network (containing independent voltage and current sources), may be replaced by a constant current source  $I_N$  in parallel with a resistance  $R_N$ , where  $I_N$  is the current flowing through a short circuit placed across the terminals and  $R_N$  is the equivalent resistance of the network as seen from the two terminals with all sources replaced by their internal resistance.

### 5.7 APPLICATION OF NORTON'S THEOREM

The procedure for the application of Norton's theorem is as follows :


1. Remove the external load  $R_L$  and then short-circuit the load terminals  $a-b$  with respect to which the Norton equivalent circuit is desired;
2. Determine the current through the terminals when they are short-circuited. This current is  $I_N$  or  $I_{SC}$ .

There is alternative method of determining  $I_N$ .

$$I_N = \frac{V_{Th}}{R_{Th}}$$

3. Redraw the network with each ideal voltage source replaced by a short circuit and each ideal current source replaced by an open circuit.
4. Calculate the resistance  $R_N$  of the redrawn network at the open-circuited terminals  $a-b$ . It is to be noted that  $R_N = R_{Th}$ .
5. Draw the Norton equivalent circuit between the terminals  $a-b$  by connecting the current source  $I_N$  in parallel with  $R_N$ .
6. The external load  $R_L$  that was short-circuited in step 1 is now reconnected across the Norton terminals  $a-b$ . It is to be noted that the direction of  $I_N$  is such that it circulates the current in the load  $R_L$  in the same direction as the original circuit circulated it.
7. The load current  $I_L$  through  $R_L$  is calculated from the formula


$$I_L = \frac{R_N}{R_N + R_L} I_N$$

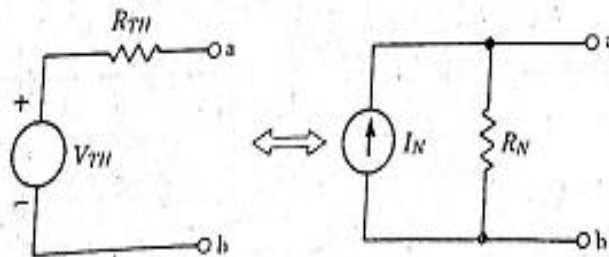

Q. 8 Determine the current through  $2\Omega$  resistor in the network by using Norton's theorem.

Soln

Step-1

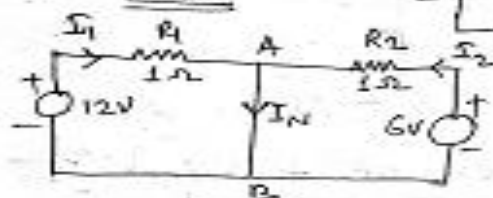

According to Norton theorem the terminal AB is short circuited.

Step-2 Determination of Norton current ( $I_N$ )

Norton current  $I_N$  is the current through AB when they are short circuited. So  $I_N$  is known as short circuit current through AB branch.

By apply KVL in the left hand mesh,

$$12 - I_1 R_1 = 0 \Rightarrow 12 - 1 \times I_1 = 0$$

$$\boxed{I_1 = 12 \text{ A}}$$

Apply KVL to the right hand mesh,

$$6 - I_2 R_2 = 0 \Rightarrow 6 - I_2 \times 1 = 0$$

$$\boxed{I_2 = 6 \text{ A}}$$

By KCL at node A  $\Rightarrow I_N = I_1 + I_2 = 12 + 6$


$$\Rightarrow \boxed{I_N = 18 \text{ Amp}}$$

Step-3 :- Calculate  $R_N$  :-

The two terminals A and B are taken out, so  
Norton resistance  $\Rightarrow R_N = R_{AB}$

$$R_N = R_1 \parallel R_2 = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{1 \times 1}{1 + 1} = 0.5 \Omega$$

Step-4 - Norton equivalent network

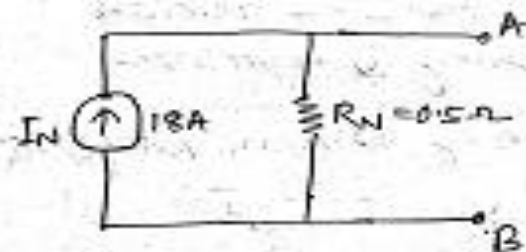


The Norton equivalent network between terminal AB is drawn by connecting the

current source  $I_N$  in parallel with  $R_N$ .

Step-5 Determination of current through  $2 \Omega$  resistor.

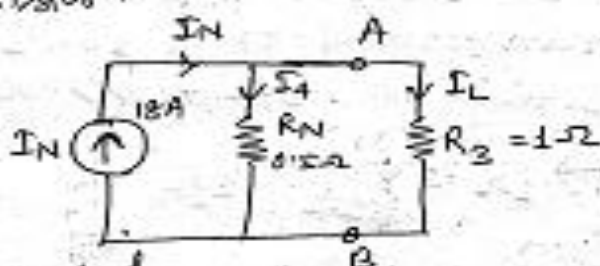The load resistor  $R_3$  that was removed in step-4 but now it is connected across the Norton's terminals AB.




By the current division rule

$$I_L = \frac{R_N}{R_N + R_3} \cdot I_N = \frac{0.5 \times 18}{0.5 + 2}$$


$$I_L = 3.6 \text{ Amp}$$

Q.10

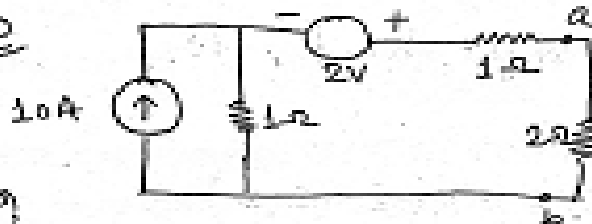

Determine the voltage across  $2\Omega$  resistor by using Norton's Theorem.

Sol<sup>n</sup>

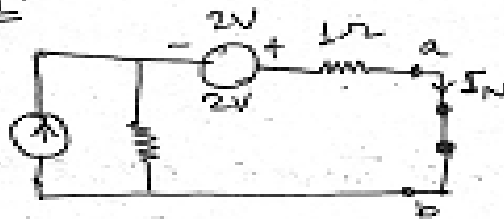

Step-1 :- The  $2\Omega$  resistor across which voltage is to be calculated and it is short-circuited in that branch.


Step-2 Determination of Norton current ( $I_N$ )

① Only  $10A$  current source with ckt. The  $2V$  voltage source is short-circuited, so by current division rule -

$$I_{N1} = \frac{1}{1+1} \times 10 = 5A$$

② Only  $2V$  voltage source in the ckt.


The  $10A$  current source is open-ckt.

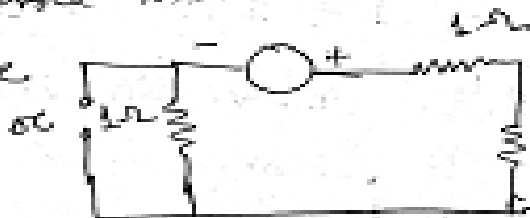

Apply the current division rule

$$I_{N2} = \frac{1}{1+1} \times 10 = 5A$$

③ Only  $2V$  voltage source in the ckt.

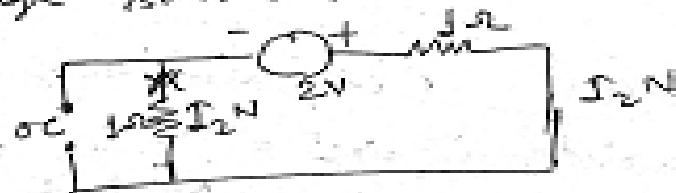

By applying KVL for this fig.

$$-I_{2N} \times 1 + 2 - I_{2N} \times 1 = 0$$

$$I_{2N} = 1A$$

But the currents ~~are~~ are flowing in same direction by superposition principle -

$$I_N = I_{1N} + I_{2N} = 5 + 1 = 6A$$


$$I_N = 6A$$

Step-3 Determination of  $R_N$  (Norton resistance)


The 10A current source is ~~open~~ or and 2V voltage source is short ckt. and load is removed

$R_N =$  resistance between terminal a-b.


Step 4

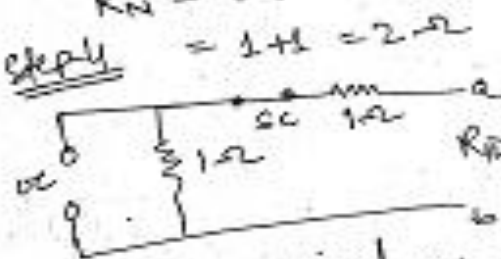

$$R_{eq} = 2\Omega$$

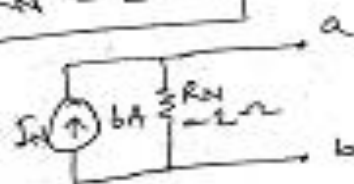

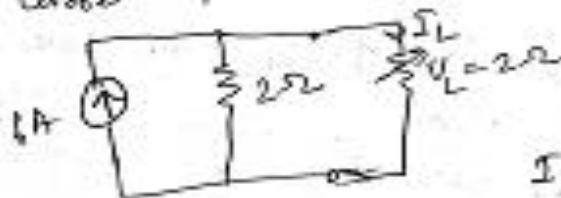In this terminal a-b is drawn by connecting the current source  $I_N$  is parallel with  $R_N$  so



Step-5


$$I_L = \frac{2}{2+2} \times 2$$

$$I_L = 3A$$


$$V_{at\ 2\Omega} = I_L R_L \Rightarrow V_L = I_L R_L = 3 \times 2 = 6$$

$$V_L = 6V$$

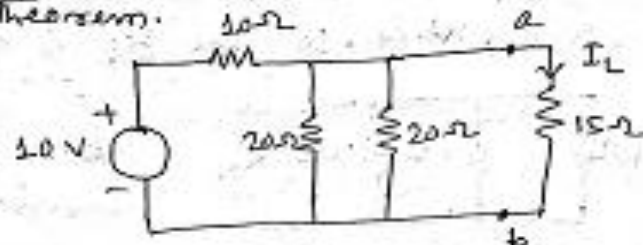Q-13 Determine the current  $I_L$  through  $15\Omega$  resistor in the given ckt. by Norton's Theorem.




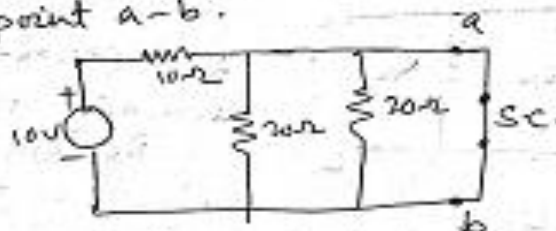Sol<sup>n</sup> Step 1 Determine the current through  $15\Omega$  resistor. So we have to remove the  $15\Omega$  resistor from the original network and short ckt. to the point a-b.




Step-2

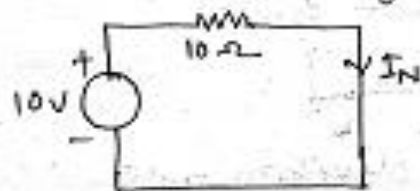Determination of Norton's Current ( $I_{sc}$ )  
The resistance of S.C. is zero. So the equivalent resistance of the two resistors of  $20\Omega$  each and S.C. is zero. So the fig will be.



$$\text{So } I_N = I_{sc} = \frac{10}{10} = 1 \text{ A.}$$


Norton Current = 1 A.

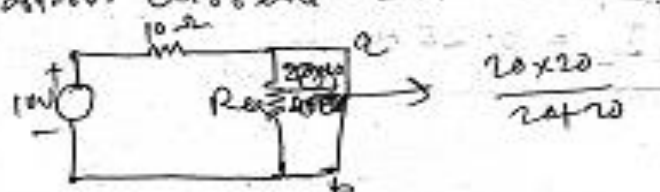

$$\frac{20 \times 20}{20 + 20}$$

Step-3 Determination of Norton's resistance

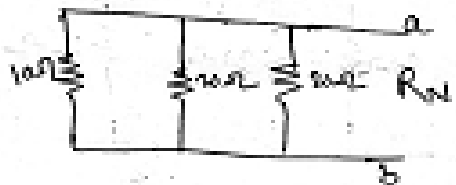Now the 10V voltage source ( $R_N$ ) is short circuited. so the fig is reduced to



As so the equivalent resistance of ckt. is

$$\frac{1}{R_N} = \frac{1}{5} \Rightarrow R_N = 5\Omega$$

Step-4


Norton's equivalent ckt.



It is parallel to  $R_N$  according to Norton's theorem.

Step-5

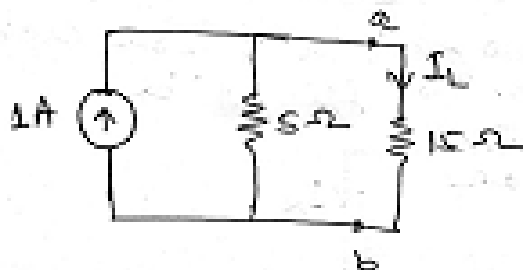Determination of current through  $15\Omega$  resistor. so the fig. will be




By current division rule

$$I_L = \frac{5}{5+15} \times 1 = 0.25 \text{ A.}$$

$$I_L = 0.25 \text{ A}$$
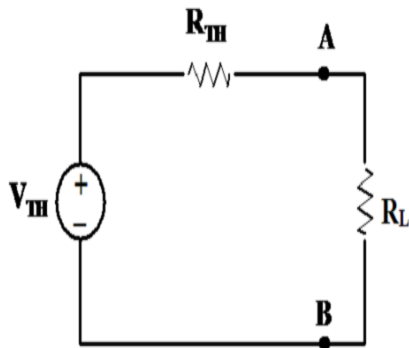
### MAXIMUM POWER TRANSFER THEOREM:

- The maximum power transferred from the power source to the load is when the resistance of the load  $R_L$  is equal to the equivalent or input resistance of the power source ( $R_{in} = R_{Th}$  or  $R_N$ ).
- The process used to make  $R_L = R_{in}$  is called impedance matching.



$$I = \frac{V_{TH}}{R_{TH} + R_L}$$

$$P_L = I^2 R_L = \frac{V_{TH}^2 R_L}{(R_{TH} + R_L)^2}$$


$$\text{For } P_L \text{ to be maximum, } \frac{dP_L}{dR_L} = 0$$

$$\text{Or, } R_L = R_{TH}$$

$$\text{So, Maximum power drawn by } R_L = I^2 R_L = \frac{V_{TH}^2 R_L}{(2R_L)^2} = \frac{V_{TH}^2}{4R_L}$$

$$\text{Power supplied by the source} = \frac{V_{TH}^2}{(R_{TH} + R_L)}$$


Q-11

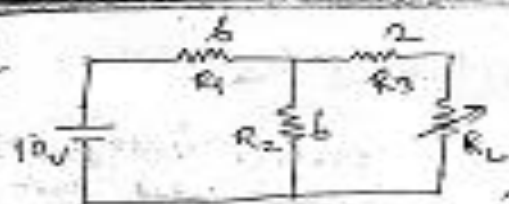

In this network determine (a) the value of the load resistance to give maximum power transfer (b) power delivered to the load.

Sol<sup>n</sup> In order to determine maximum power transfer, we have to determine its Thevenin equivalent network

Step 1 Determination of  $V_{th}$

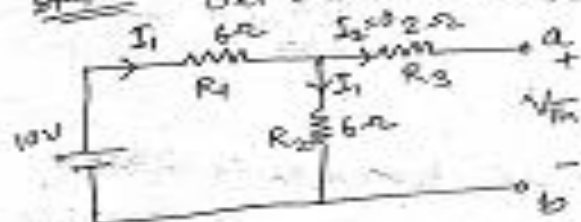

Disconnect the load resistance  $R_L$  from original network. Now the ckt. is open between

terminal a-b, there is no current through  $R_3$  and the current through  $R_1$  &  $R_2$  is same. By KVL to the left hand mesh,

$$10 - I_1 R_1 - I_1 R_2 = 0 \Rightarrow I_1 = \frac{5}{6} \text{ A}$$


Now KVL to the right hand mesh

$$I_1 R_2 - I_2 R_3 - V_{th} = 0 \Rightarrow \frac{5}{6} \times 6 - 0 \times 2 - V_{th} = 0$$


$$V_{th} = 6 I_1 \Rightarrow V_{th} = 6 \times \frac{5}{6} = 5 \text{ A}$$

$$\boxed{V_{th} = 5 \text{ A}}$$

Step-2 Determination of  $R_{th}$

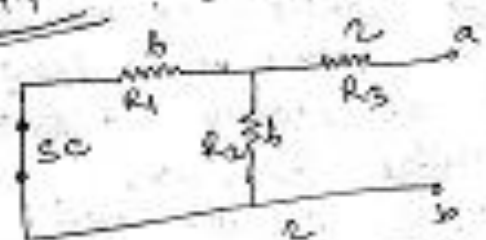

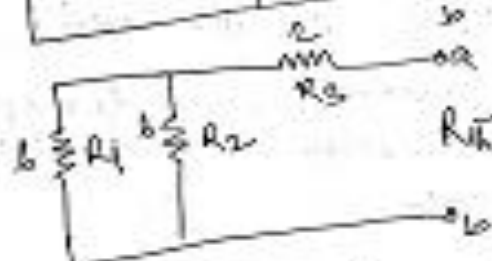The 10V voltage source is short circuited. Now the fig can be redrawn as



$$\begin{aligned} R_{th} &= R_1 \parallel R_2 + R_3 \\ &= \frac{R_1 \times R_2}{R_1 + R_2} + R_3 \\ &= \frac{6 \times 6}{6 + 6} + 2 \end{aligned}$$

$$R_{th} = 5 \Omega$$

For maximum power transfer of CRT-6


$$R_L = R_{th} = 5 \Omega$$

$$P_{L \max} = I_L^2 R_{th} = \left( \frac{V_{th}}{R_{th} + R_{th}} \right)^2 \times R_{th}$$

$$= \frac{V_{th}^2}{4 R_{th}} = \frac{5^2}{4 \times 5} = 1.25 \text{ W}$$

$$P_{L \max} = 1.25 \text{ W}$$

## Star-Delta Transformation

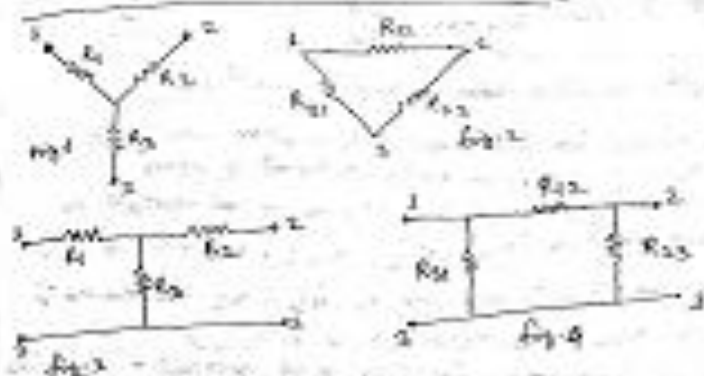

From above fig (1) and (2)

The resistance between terminal 1 and 2 for star network = resistance between terminal 1 and 2 for delta network

$$R_1 + R_2 = R_{12} + (R_{23} + R_{31})$$

$$R_1 + R_2 = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (1)}$$

Similarly, the resistance between terminal 2 & 3 for star network = resistance between terminal 2 & 3 for delta network

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}}$$

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

Similarly, the resistance between the terminal 3 and 1 for star network = resistance between terminal 3 & 1 for delta network

$$R_3 + R_1 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$

$$R_3 + R_1 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (3)}$$

### Delta to Star Transformation

To convert the delta network to star network, it is necessary to express each element of star network ( $R_1, R_2, R_3$ ) in terms of the element of delta network ( $R_{12}, R_{23}, R_{31}$ ). Equation (1) to (3) can be used to find out  $R_1, R_2$  &  $R_3$  in terms of  $R_{12}, R_{23}, R_{31}$ . Addition of all equations (1), (2) & (3) and division of the result by 2 gives

$$R_1 + R_2 + R_3 = \frac{R_{12}R_{23} + R_{23}R_{31} + R_{31}R_{12}}{R_{12} + R_{23} + R_{31}}$$

Subtraction of eqn (2) from eqn (1)  $\Rightarrow$  --- (3)

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

Subtraction of eqn (3) from eqn (1)  $\Rightarrow$

$$R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

Subtraction of eqn (1) from eqn (3)  $\Rightarrow$

$$R_3 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

Star resistance =  $\frac{\text{Product of adjacent delta resistances}}{\text{Sum of delta resistances}}$

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

### Star to delta Transformation :->

Delta-connected resistances can be converted in terms of star connected resistances. For we have to find  $R_{12}$ ,  $R_{23}$  and  $R_{31}$  in terms of  $R_1$ ,  $R_2$  and  $R_3$ . From the eqn. (1), (2) and (3)

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_1^2 R_{23} R_3 + R_{23}^2 R_1 R_2 + R_3^2 R_1 R_2}{(R_2 + R_{23} + R_3)^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{23} R_3 R_1}{R_2 + R_{23} + R_3} \quad \text{--- (4)}$$

Division of eqn. (4) by eqn. (1) we get

$$R_{12} = \frac{1}{R_3} (R_1 R_2 + R_2 R_3 + R_3 R_1)$$

$$R_{12} = \frac{\sum R_1 R_2}{R_3} \quad \text{--- (5)}$$

where  $\sum R_1 R_2 = R_1 R_2 + R_2 R_3 + R_3 R_1$

Divide the eqn. (4) by eqn. (2) we get

$$R_{23} = \frac{1}{R_1} (R_1 R_2 + R_2 R_3 + R_3 R_1)$$


$$R_{23} = \frac{\sum R_1 R_2}{R_1} \quad \text{--- (6)}$$

Divide the eqn. (4) by eqn. (3) we get

$$R_{31} = \frac{1}{R_2} (R_1 R_2 + R_2 R_3 + R_3 R_1)$$


$$R_{31} = \frac{\sum R_1 R_2}{R_2} \quad \text{--- (7)}$$

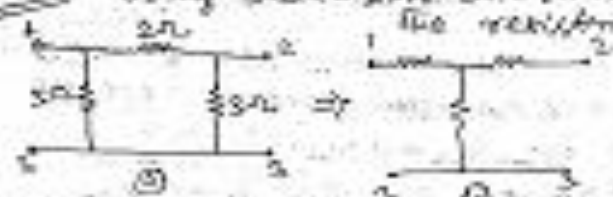Q.12 Using Delta-Star conversion, find the resistances of network



② Delta to star Transformation

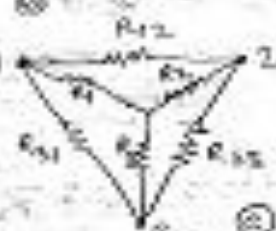the superimposed delta and star network are shown in fig ③



$$\sum R_{\Delta} = R_{12} + R_{23} + R_{31} = 2 + 3 + 5 = 10 \Omega$$

$$R_1 = \frac{R_{12} R_{31}}{\sum R_{\Delta}} = \frac{2 \times 5}{10} = 1 \Omega$$

$$R_2 = \frac{R_{12} R_{23}}{\sum R_{\Delta}} = \frac{2 \times 3}{10} = 0.6 \Omega$$

$$R_3 = \frac{R_{23} R_{31}}{\sum R_{\Delta}} = \frac{3 \times 5}{10} = 1.5 \Omega$$

③ star to delta Transformation

$$\sum R_1 R_2 = R_1 R_2 + R_2 R_3 + R_3 R_1 = 3 \Omega$$

$$R_{12} = \frac{\sum R_1 R_2}{R_3} = \frac{3}{1.5} = 2 \Omega$$


$$R_{23} = \frac{\sum R_1 R_2}{R_1} = \frac{3}{1} = 3 \Omega$$

$$R_{31} = \frac{\sum R_1 R_2}{R_2} = \frac{3}{0.6} = 5 \Omega$$

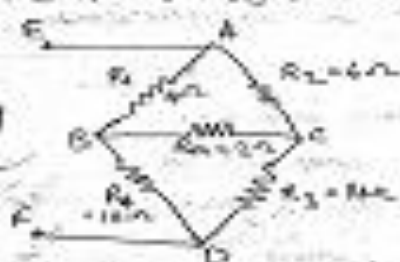Q.14. Find the resistance between the terminals E-F of the bridge circuit given in below fig. by using delta-star transformation.

Sol<sup>n</sup>

Here the two delta triangles are connected to each other by common impedance  $2\Omega$ .



We will transform the delta network of terminals A, B, C to star network.

In star connection,  $R_A = \frac{R_1 R_2}{\sum R_0}$

$$\sum R_0 = R_1 + R_2 + R_m = 4 + 6 + 2 = 12\Omega$$

$$\boxed{\sum R_0 = 12\Omega}$$

$$R_A = \frac{R_1 R_2}{\sum R_0} = \frac{4 \times 6}{12}$$

$$\boxed{R_A = 2\Omega}$$

$$R_B = \frac{R_1 \times R_m}{\sum R_0} = \frac{4 \times 2}{12} = \frac{2}{3}\Omega$$


$$\boxed{R_B = \frac{2}{3}\Omega}$$

$$R_C = \frac{R_2 \times R_m}{\sum R_0} = \frac{6 \times 2}{12} = 1\Omega$$

$$\boxed{R_C = 1\Omega}$$

After the completion of Delta to star transformation, the bridge ckt. will be reconstructed as.

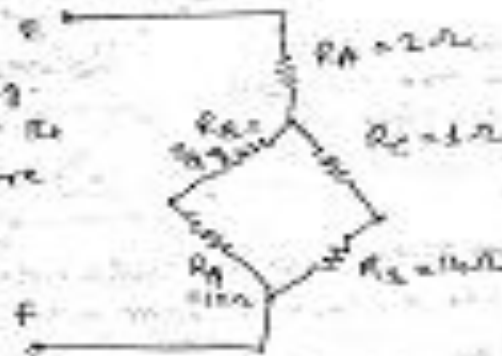From this fig. we shall get the  $R_2$  and  $R_3$  are in series connected.



So the total resistance  $R_5 = R_2 + R_3 = 1 + 14 = 15\Omega$


$$R_5 = 15\Omega$$

Similarly  $R_6$  and  $R_4$  are in series connected. So the total resistance

$$R_6 = R_3 + R_4 = \frac{2}{3} + 10$$

$$R_6 = \frac{32}{3}\Omega$$

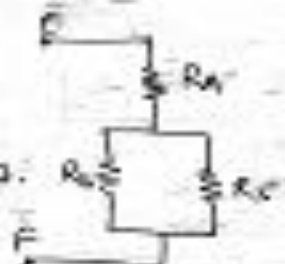From final fig. we shall conclude that  $R_5$  is parallel to  $R_6$  and the output  $R_A$  is series connected. So the total resistance between ef is  $R_{EF}$



$$R_{EF} = R_A + \frac{R_5 \times R_6}{R_5 + R_6} = 2 + \frac{15 \times \frac{32}{3}}{15 + \frac{32}{3}} = 8.234\Omega$$

$$R_{EF} = 8.234\Omega$$

End