

**DEPARTMENT OF ELECTRICAL ENGINEERING  
GOVERNMENT COLLEGE OF ENGINEERING  
KALAHANDI  
BHAWANIPATNA**



**Lecture Notes on Basic Electronics**

**By**

**Dr. Deepa Das**

**Assistant Professor**

**Department of Electrical Engineering**

## **Disclaimer**


This document does not claim any originality and cannot be used as a substitute for prescribed textbooks. The information presented here is merely a collection by the committee members for their respective teaching assignments. Various sources such as text books, reference books as well as freely available materials from internet were consulted for preparing this document. The ownership of the information lies with the respective author or the institution. Further, this document is not intended to be used for commercial purpose.

Def. An operational amplifier or op-amp is a very high gain differential amplifier with high input impedance and low output impedance.

→ The word operational stands for various mathematical operations such as addition, subtraction, multiplication, differentiation, integration, etc and amplifier is one which boosts or amplifies the signal. Since this circuit performs both mathematical operations and amplification, it is called operational amplifier (Op-amp).


Application :- Voltage amplitude changes (amplitude and polarity), Oscillators, filter circuits and many types of instrumentation circuits.

Basic opamp

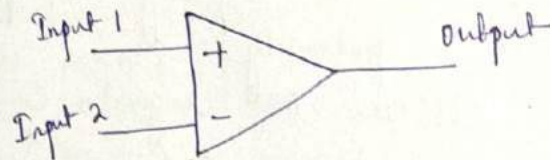


Single-Ended Input

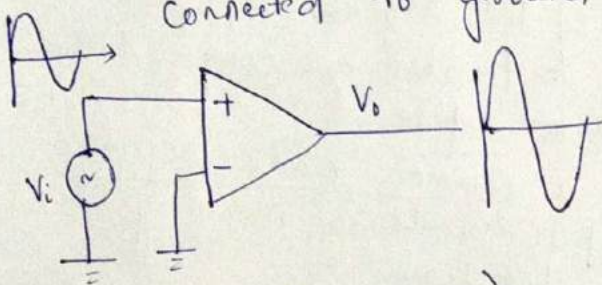→ Single-ended input operation means when the input is connected to one input with the other input connected to ground.




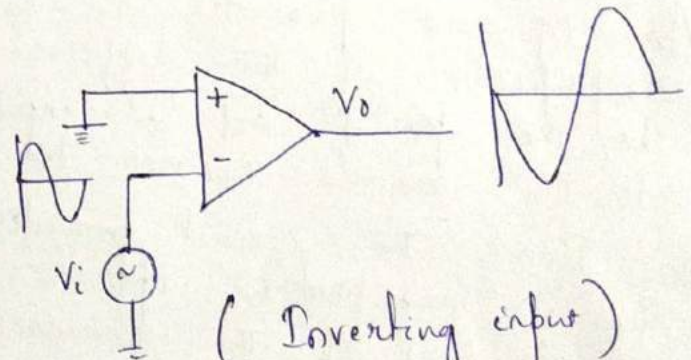(Non-inverting input)  
(The input is applied to the (+) input)



(Inverting input)  
(The input is applied to the (-) input)

Double-Ended (Differential) Input :-

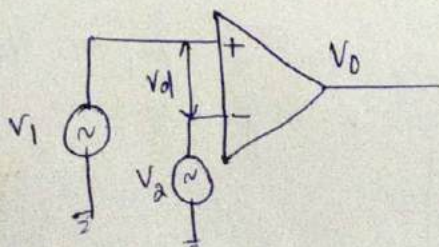



$V_1$  = Non-inverting input  
 $V_2$  = Inverting input  
 $A$  = voltage gain

The differential input is


$$V_{id} \text{ or } V_d = V_1 - V_2$$

Output voltage  $V_{out} = A V_{id} = A (V_1 - V_2)$

Double-Ended Output :-

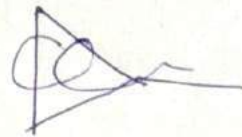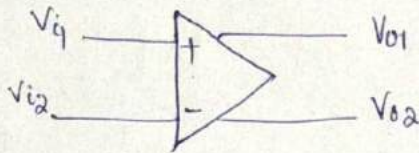

Common-Mode Operation

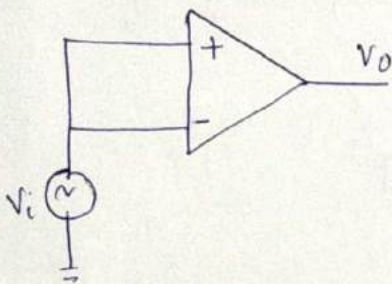

When the same input signals are applied to both inputs, the signals are equally amplified but in opposite polarity signals at the output. Hence the signals cancel.

$$V_{out} = A (V_1 - V_2) = A \cdot 0 = 0 \quad (V_1 = V_2)$$

\* But, practically  $V_{out}$  is very small.

Differential and Common mode operations :-

→ An op-amp provides an output component due to the amplification of the difference of the signals applied to the (+) and (-) inputs and also a component due to the signals common to both inputs.

→ Since the circuit provides a common mode rejection that is amplification of the opposite input signals is much greater than that of the common input signals. This is called the common-mode rejection ratio (CMRR).

\* Differential Inputs :- When separate inputs are applied to the Op-amp, the resulting signal is

$$V_d = V_{i1} - V_{i2}$$

\* Common Inputs :- When both input signals  $V_{i1}$  and  $V_{i2}$  are the same, the resulting signal is

$$V_c = \frac{1}{2} (V_{i1} + V_{i2})$$

\* Output voltage :- Since any signals applied to an op-amp have both in-phase and out-of-phase components, the resulting output is

$$V_o = A_d V_d + A_c V_c$$

$V_d$  = difference voltage

$V_c$  = common voltage

$A_d$  = Differential gain of the amplifier

$A_c$  = Common-mode gain of the amplifier.

\* Opposite Polarity Inputs :-

when  $V_{i1} = -V_{i2} = V_s$

Then  $V_d = V_{i1} - V_{i2} = V_{i1} - (-V_{i2}) = 2V_s$

$$V_c = \frac{1}{2} (V_{i1} + V_{i2}) = \frac{1}{2} (V_{i1} - V_{i1}) = 0V$$

Hence  $V_o = 2A_d V_s$

\* Same polarity Inputs :-

When  $V_{i1} = V_{i2} = V_s$

Then  $V_d = V_{i1} - V_{i2} = V_s - V_s = 0$

$$V_c = \frac{1}{2} (V_{i1} + V_{i2}) = \frac{1}{2} (V_s + V_s) = V_s$$

Then  $V_o = A_c V_s$

\* Common-mode Rejection Ratio

→ A measure of rejection of signals common to both inputs is referred to as the common-mode rejection of the amplifier and the numerical value is known as Common-mode rejection ratio (CMRR).

→ It is defined as the ratio of differential voltage gain to common-mode voltage gain and it is given as

$$CMRR = \frac{A_d}{A_c}$$

In an ideal differential amplifier, the output signal  $V_{out}$  is

$$V_{out} = A(V_{i1} - V_{i2}) = A V_d$$

But practically,  $V_{out} = A_d V_d + A_c V_c$

Where  $V_d = V_{i1} - V_{i2}$

$$V_c = \frac{1}{2}(V_{i1} + V_{i2})$$

Let the output voltage  $V_{out}$  is expressed as a linear combination of two input voltages  $V_{i1}$  and  $V_{i2}$ .

Then

$$\begin{aligned} V_{i1} &= V_c + \frac{1}{2} V_d \\ V_{i2} &= V_c - \frac{1}{2} V_d \end{aligned}$$

Then  $V_{out} = A_1 V_{i1} + A_2 V_{i2}$

Where  $A_1 \rightarrow$  the voltage gain for input  $V_{i1}$  with  $V_{i2}$  is grounded.

$A_2 \rightarrow$  voltage gain for input  $V_{i2}$  with  $V_{i1}$  is grounded.

Solving  $V_d$  and  $V_c$  for  $V_{i1}$  and  $V_{i2}$  is

$$V_{i1} = V_c + \frac{1}{2} V_d$$

$$V_{i2} = V_c - \frac{1}{2} V_d$$

Substituting these values in  $V_{out}$

$$\begin{aligned} V_{out} &= A_1 \left( V_c + \frac{1}{2} V_d \right) + A_2 \left( V_c - \frac{1}{2} V_d \right) \\ &= \frac{1}{2} (A_1 - A_2) V_d + (A_1 + A_2) V_c \\ &= A_d V_d + A_c V_c \end{aligned}$$

Where  $A_d = \frac{A_1 - A_2}{2}$

$$A_c = (A_1 + A_2)$$

$$\boxed{CMRR = \frac{A_d}{A_c}}$$

$$\boxed{CMRR(\log) = 20 \log \frac{A_d}{A_c}}$$

$$V_0 = A_d V_d + A_c V_c = A_d V_d \left( 1 + \frac{A_c V_c}{A_d V_d} \right) \quad (3)$$


$$V_0 = A_d V_d \left( 1 + \frac{1}{\text{CMRR}} \frac{V_c}{V_d} \right)$$

Hence, it is clearly shown that even when both  $V_d$  and  $V_c$  components of signals are present, for large values of CMRR, the output voltage will be mostly due to the difference signal.

### Ideal Op-amp :- Characteristics

- The op-amp is said to be ideal having the following characteristics
- Its open-loop gain  $A$  is  $\infty$ .
- Its input resistance (i.e. the resistance measured between inverting and non-inverting terminal)  $R_{in}$  is  $\infty$ .
- Its output impedance  $R_{out}$  is 0.
- Infinite frequency bandwidth.
- Drift of characteristics with temperature is nil.
- CMRR is  $\infty$ .
- Slew rate is  $\infty$ .


### Basic Op-amp

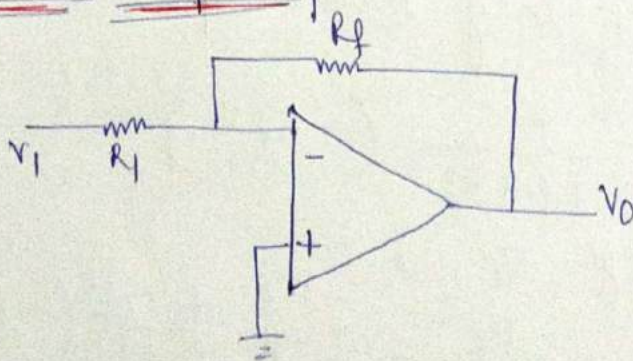

(The resulting output is opposite in phase to the input signal.)


(Basic op-amp connection)

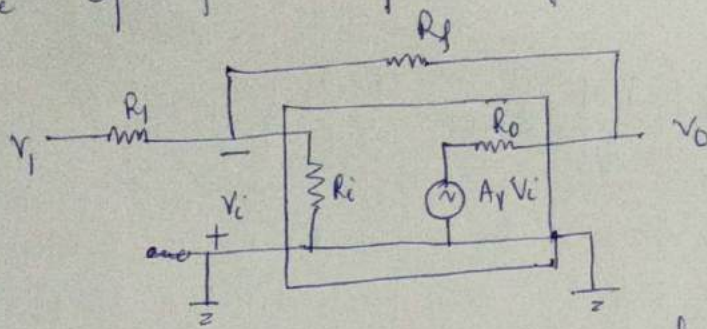If the op-amp is replaced by its ac equivalent circuit -



(op-amp ac equivalent circuit)

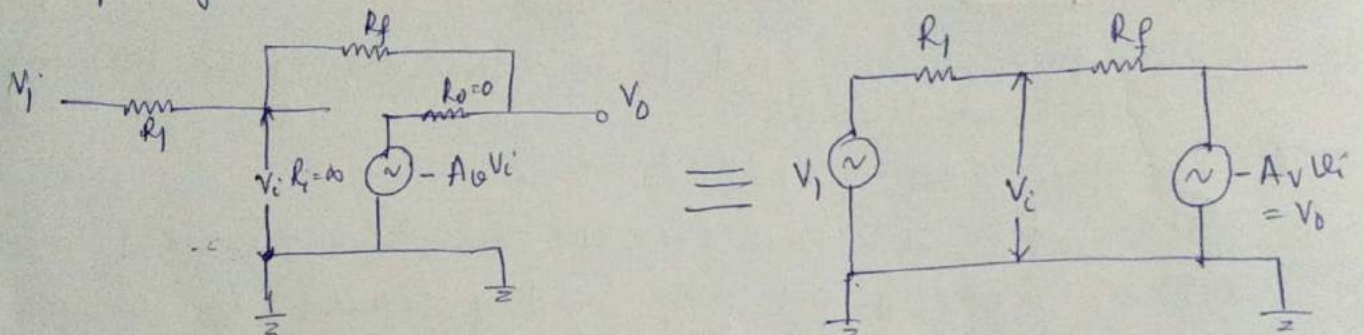Replacing  $R_i = \infty$  and  $R_o = 0$ .



(ideal op-amp circuit)

Using superposition theorem for solving  $V_i$  in terms of the components making  $-A_V V_i$  set to zero.

$$V_{i1} = \frac{R_f}{R_1 + R_f} V_1$$

For the source  $-A_V V_i$  only making  $V_1$  set to zero

$$V_{i2} = \frac{R_1}{R_1 + R_f} (-A_V V_i)$$

Hence, the total voltage  $V_i$  is

$$V_i = V_{i1} + V_{i2} = \frac{R_f}{R_1 + R_f} V_1 + \frac{R_1}{R_1 + R_f} (-A_V V_i)$$

$$\Rightarrow \left( 1 + \frac{R_1}{R_1 + R_f} A_V \right) V_i = \frac{R_f}{R_1 + R_f} V_1$$

$$\Rightarrow \left( \frac{R_1 + R_f + R_1 A_V}{R_1 + R_f} \right) V_i = \frac{R_f}{R_1 + R_f} V_1$$

$$V_i = \frac{R_f}{R_f + (1 + A_v)R_1} V_1$$

(4)

if  $A_v \gg 1$ , hence  $A_v R_1 \gg (1 + R_f)$ .

So

$$V_i = \frac{R_f}{A_v R_1} V_1$$

So,

$$\frac{V_o}{V_i} = \frac{-A_v V_i}{R_f V_i} \cdot \frac{A_v R_1 \cdot \frac{R_f}{A_v R_1} V_1}{A_v R_1}$$

$$= \frac{-A_v V_i}{R_f V_i} = \frac{-A_v}{R_f} \frac{R_f V_1}{A_v R_1}$$

$$\Rightarrow \frac{V_o}{V_i} = - \frac{R_f}{R_1} \cdot \frac{V_1}{V_i}$$

$$\Rightarrow \boxed{\frac{V_o}{V_1} = - \frac{R_f}{R_1}}$$

Hence,  $V_o = \left( - \frac{R_f}{R_1} \right) V_1$

depends on only  $R_f$  and  $R_1$ .

Unity gain

if  $R_f = R_1$ , then


$$\boxed{\frac{V_o}{V_1} = - \frac{R_f}{R_1} = -1}$$

The circuit provides a unity voltage gain with  $180^\circ$  phase inversion.

### Virtual Ground

Virtual ground is making a node on a connection virtually ground i.e. it is not physically connected to the ground but voltage at that point/node is 0V. Therefore, it is referred as ground.

Eq

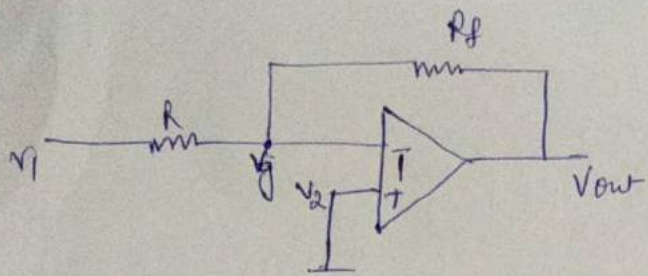

(inverting amplifier)

In an ideal op-amp open loop gain  $A$  is  $\infty$ .

$$A = \frac{V_{out}}{(v_2 - v_1)} = \frac{V_{out}}{(V_{noninv} - V_{inv})}$$

if  $A = \infty$ ,  $v_1 - v_2 = 0$

As  $v_2$  is connected to ground  $v_2 = 0$ , hence  $v_1 = 0$

Though  $v_1$  is not connected to the ground, ~~so~~  $v_1 = 0$ .

In the practical op-amp, the gain is very very large.

Let  $A = 10^5$ .

The output voltage  $V_{out}$  is to be limited to the supply voltage  $V_{cc}$ , which is of the order 10 or 15 V.

Then

$$V_{in} = (V_{noninv} - V_{inv}) = \frac{V_{out}}{10^5} = \frac{10}{10^5} = 0.0001 \text{ V}$$

Hence


$$V_{noninv} - V_{inv} = 0.0001 \text{ V} \approx 0$$

As  $v_2 = V_{noninv} = 0$  Hence, there is a virtual short in between noninverting input and inverting input.

# Practical OP-amp Circuits
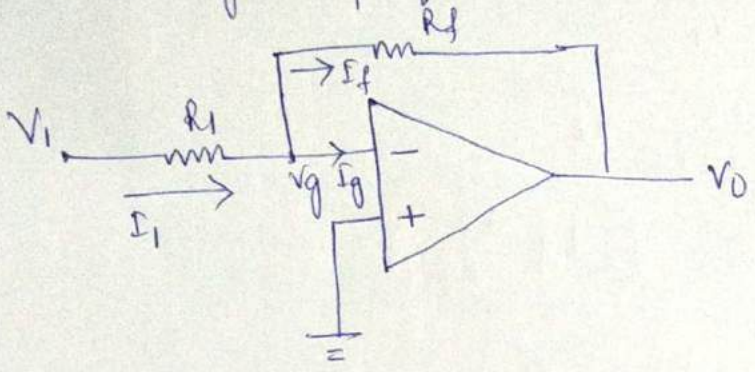
## 1) Inverting Amplifier :-

It is the most widely used constant-gain amplifier circuit.



As we know  

$$V_o = -A_d V_g$$

$$\Rightarrow V_g = -\frac{V_o}{A_d}$$

(Inverting constant-gain multiplier)

For ideal op-amp  $A_d = \infty$ , hence  $V_g = 0$   
 So  $I_g = \frac{V_g}{R_i} = \frac{V_g}{\infty} = 0$  ( $\because$  for ideal opamp  $R_i = \infty$ )

Applying KCL at the node



$$I_1 = I_g + I_f$$

$$\Rightarrow \frac{V_i - V_g}{R_1} = 0 + \frac{V_g - V_o}{R_f}$$

$$\Rightarrow \frac{V_i}{R_1} = -\frac{V_o}{R_f} \Rightarrow \boxed{\frac{V_o}{V_i} = -\frac{R_f}{R_1}}$$

The output is inverted from the input.

## 2) Non Inverting Amplifier :-

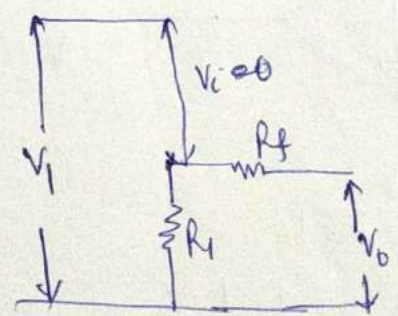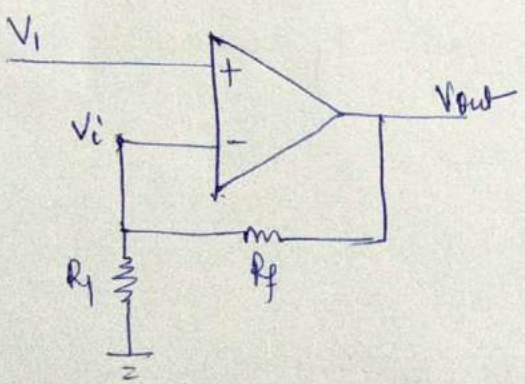

(Non inverting constant-gain multiplier)

(Equivalent circuit)

From the potential divider network

$$V_i = \frac{R_1}{R_1 + R_f} v_o$$

As  $I_g = 0$   $\hat{=}$  virtual ground  
 ~~$V_i = V_1$~~   $V_i = V_1$


$$\Rightarrow \text{Hence } V_1 = \frac{R_1}{R_1 + R_f} v_o$$

$$\Rightarrow \frac{v_o}{v_1} = \frac{R_1 + R_f}{R_1} = \left( 1 + \frac{R_f}{R_1} \right)$$


$$\Rightarrow \boxed{v_o = \left( 1 + \frac{R_f}{R_1} \right) v_1}$$

So, the overall closed-loop gain of a non-inverting amplifier will always be greater than one.

### 3) Voltage Follower

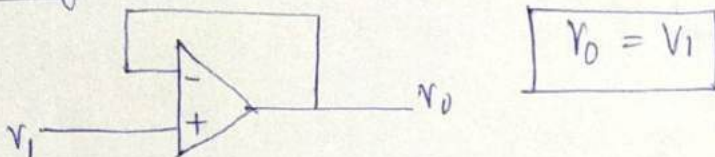

### 4) Summing Amplifier

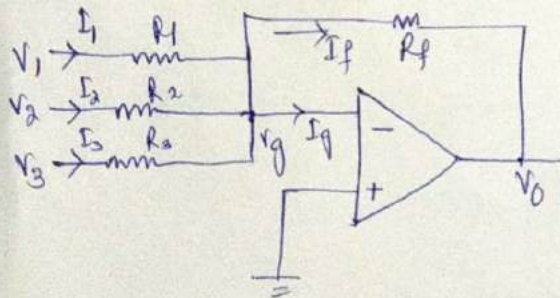

This circuit provides a algebraically summing of three voltages, each multiplied by a constant-gain factor.  
 We know that  $I_g = 0$  and  $v_g = 0$ .

Applying KCL

$$I_1 + I_2 + I_3 = I_g + I_f$$

$$\frac{v_1 - v_g}{R_1} + \frac{v_2 - v_g}{R_2} + \frac{v_3 - v_g}{R_3} = 0 + \frac{v_g - v_o}{R_f}$$

$$\Rightarrow \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = -\frac{v_o}{R_f}$$

$$\Rightarrow \boxed{v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)}$$


If  $R_1 = R_2 = R_3 = R_f$

Then  $V_0 = -(V_1 + V_2 + V_3)$

(6)

The output is the summation of the inputs.

Op-amp as Subtractor

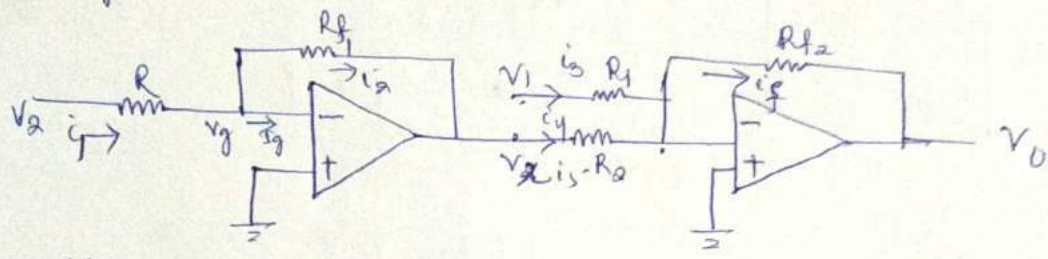

$V_g = 0$  &  $I_g = 0$

$\frac{V_2 - V_g}{R} = \frac{V_g - V_n}{R_{f1}} \Rightarrow \frac{V_2}{R} = -\frac{V_n}{R_{f1}}$

$\Rightarrow V_n = -V_2 \quad (R = R_{f1})$

Applying KCL to the second part

$i_4 + i_5 = i_f \Rightarrow \frac{V_1 - V_g}{R_1} + \frac{V_n - V_g}{R_2} = \frac{V_g - V_0}{R_{f2}}$

$\Rightarrow \frac{V_1}{R_1} + \frac{V_n}{R_2} = -\frac{V_0}{R_{f2}}$

But  $V_n = -V_2$

Replacing the same

$\Rightarrow \frac{V_1}{R_1} - \frac{V_2}{R_2} = -\frac{V_0}{R_{f2}} \Rightarrow V_0 = -\left(\frac{R_{f2}}{R_1} V_1 - \frac{R_{f2}}{R_2} V_2\right)$


if  $R_1 = R_2 = R_f$ , then

$V_0 = -(V_1 - V_2)$

Since, the output voltage is the difference of two input voltages, it is known as subtractor.
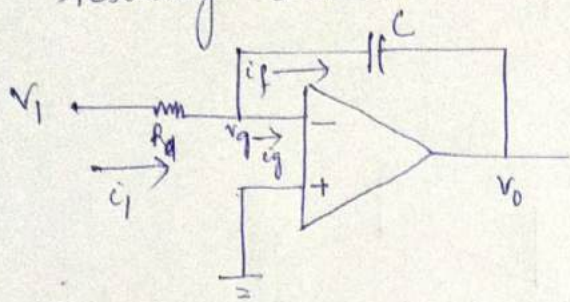
## 6) Integrator

→ If the feedback component used is a capacitor, then the resulting circuit is called an integrator.



Applying  
 $i_i = i_g + i_f$

$$\Rightarrow \frac{v_i - v_g}{R} = v_g i_g + C \frac{d(v_g - v_o)}{dt}$$

$$\Rightarrow \frac{v_i}{R} = -C \frac{dv_o}{dt} \Rightarrow \frac{dv_o}{dt} = -\frac{1}{RC} v_i$$

Integrating both sides w.r.t  $t$  we get

$$v_o(t) = -\frac{1}{RC} \int_0^t v_i(t) dt$$


$$v_o \propto \int v_i dt$$

Since the output is directly proportional to the integration of the input, it is known as integrator.

★ If more than one input is applied to an integrator, then the resulting operation is

$$v_o(t) = - \left[ \frac{1}{R_1 C} \int v_1(t) dt + \frac{1}{R_2 C} \int v_2(t) dt + \frac{1}{R_3 C} \int v_3(t) dt \right]$$

## 7) Differentiator

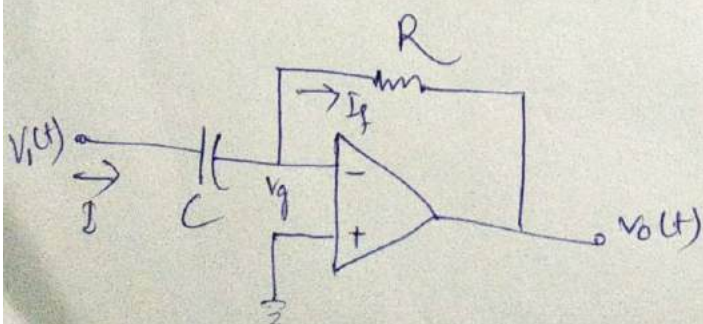

$$i_i = i_g + i_f$$

$$C \frac{d(v_i - v_g)}{dt} = \frac{v_g - v_o}{R}$$

$$\Rightarrow C \frac{dv_i}{dt} = -\frac{v_o}{R}$$

$$\Rightarrow v_o(t) = -RC \frac{dv_i(t)}{dt}$$

$$\Rightarrow v_o(t) \propto \frac{dv_i(t)}{dt}$$

(7)

Since the output voltage is proportional to the differentiation of the input, it is known as differential Amplifier.


### Some Important Op-amp Specifications.

1) Output offset voltage:- It is the dc voltage present at the output terminal when the two input terminals are grounded.

2) Input offset voltage:- It is defined as the resultant difference in voltage required at the input of op-amp to make the output voltage to zero.

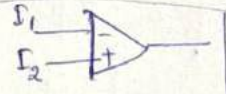3) Input offset current:- It is defined as the difference between the two currents entering the input terminals of a balanced amplifier for  $v_{out} = 0$ .

$$I_{is} (\text{offset}) = I_1 - I_2 \text{ for } v_{out} = 0$$



4) Input Bias current:- It is defined as the average of the current across the two terminals of the op-amp to make the output voltage zero.

$$I_b = \frac{I_1 + I_2}{2} \text{ for } v_{out} = 0$$

5) Input offset current drift:- It is defined as the ratio of change in input offset current to the change in temperature.

6) Input offset voltage drift:- It is defined as the ratio of change in input offset voltage to the change in temperature.

7) Slew Rate:- It is the opamp's ability to handling varying signals.


→ It is defined as the maximum rate of change of output voltage per microsecond ( $V/\mu\text{sec}$ ).

$$SR = \frac{\Delta V_o}{\Delta t} \quad \text{V}/\mu\text{sec}$$

8) Power supply rejection ratio :- It is defined as the ratio of change in output offset voltage to the change in power supply voltage

$$PSRR = \frac{\Delta V_{CO}}{\Delta V_{CC}}$$

9) Gain - Bandwidth :-

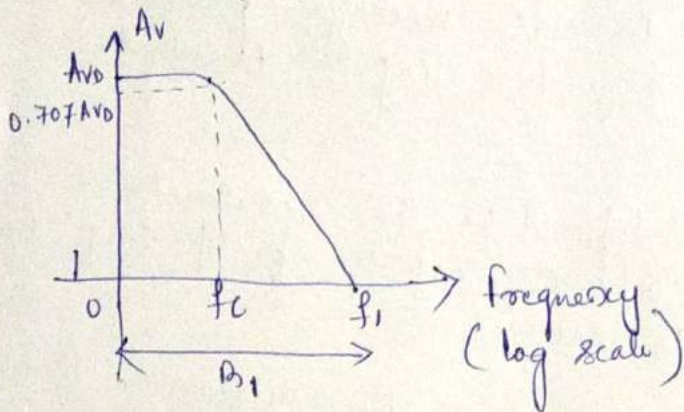

(Gain vs frequency of a typical op-amp)

As the frequency of the input signal increases the open loop gain drops off until it reaches the value of 1.

The frequency range at which this unity gain is achieved is known as unity-gain bandwidth.

The cut-off frequency of the op-amp  $f_c$  is defined as the freq frequency range, when the gain is drops by 3 db or  $0.707 A_{v0}$ .

The unity-gain frequency ( $f_1$ ) and cutoff frequency is related by

$$f_1 = A_{v0} f_c$$

Hence, the unity gain frequency ( $f_1$ ) may also be called the gain-bandwidth product of the op-amp.

## Feedback Concept :-

→ When a part or fraction of output is combined to the input, feedback is said to exist.  
The process of combining a fraction of output energy (voltage or current) back to the input is called feedback.


→ When the feedback voltage/current is applied to increase the input signal, it is called the positive/direct/regenerative feedback.

Positive feedback causes excessive distortion and instability, and hence, seldom used in amplifiers. Because of its capability of increasing the power of the original signal it is used in oscillator circuits.

→ When the feedback voltage/current is so applied to weaken the input signal, it is called negative/inverse/degenerative feedback.

Negative feedback reduces the amplifier gain but it has numerous advantages

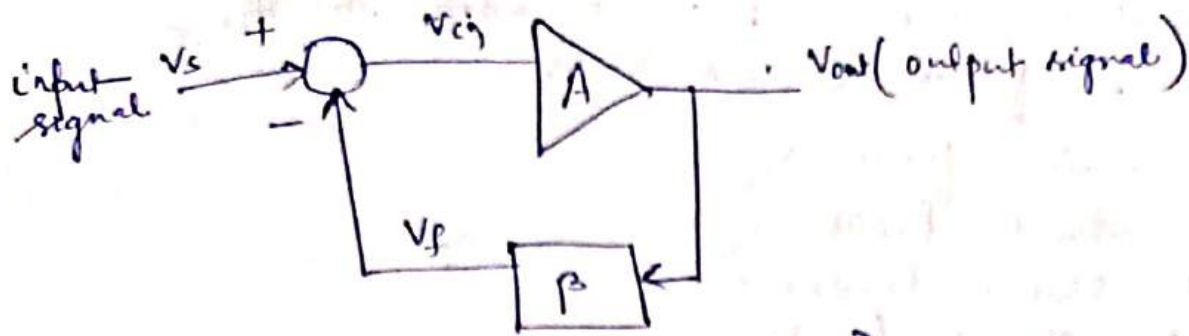- (a) Gain stability
- (b) Reduction in non-linear distortion
- (c) Reduction in noise
- (d) Improvement in frequency response
- (e) Increase in input impedance
- (f) Decrease in output impedance.







(feedback amplifier)

- ~~An amplifier with two input terminals~~
- The amplifier has a voltage gain  $A$  and output voltage  $V_{out}$  is applied to a feedback network which reduces  $V_{out}$  by a factor  $\beta$  to give a feedback voltage  $V_f$ .
- The feedback voltage  $V_f$  is in phase opposition to the input signal voltage  $V_s$ .
- The instantaneous voltage at the amplifier input terminal is  $V_{in} = V_s - V_f$ . Thus, the input voltage is less than the input signal voltage because of the negative feedback.
- The feedback amplifier essentially consists of two parts eg. an amplifier and a feedback network.
- The feedback may also be classified as voltage feedback and current feedback.
- In voltage feedback, the energy feedback to the input terminals is proportional to the output voltage.
- In current feedback, the energy feedback to the input terminals is proportional to the current through the load.

Both voltage and current can be feedback to the input either in series or in parallel resulting four basic feedback connections,

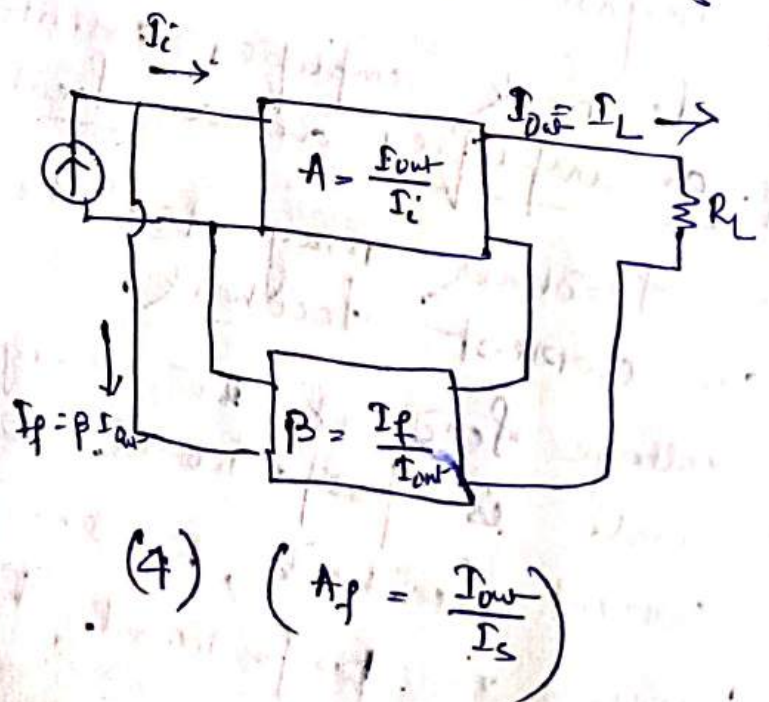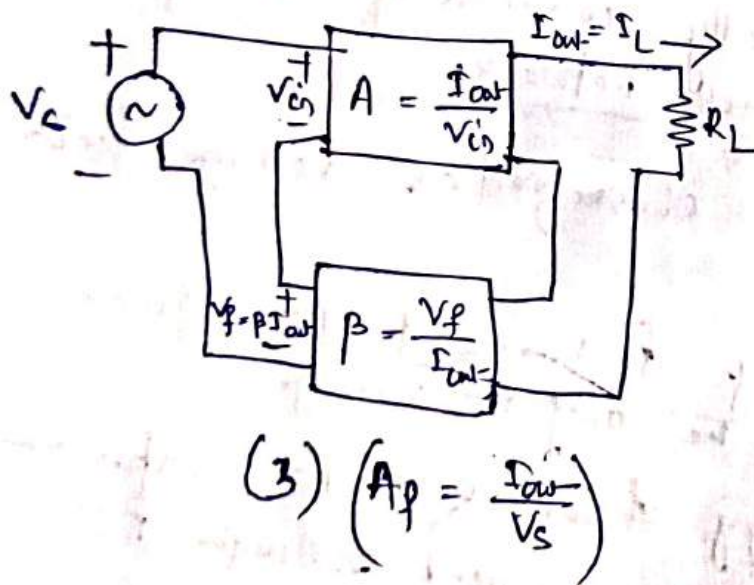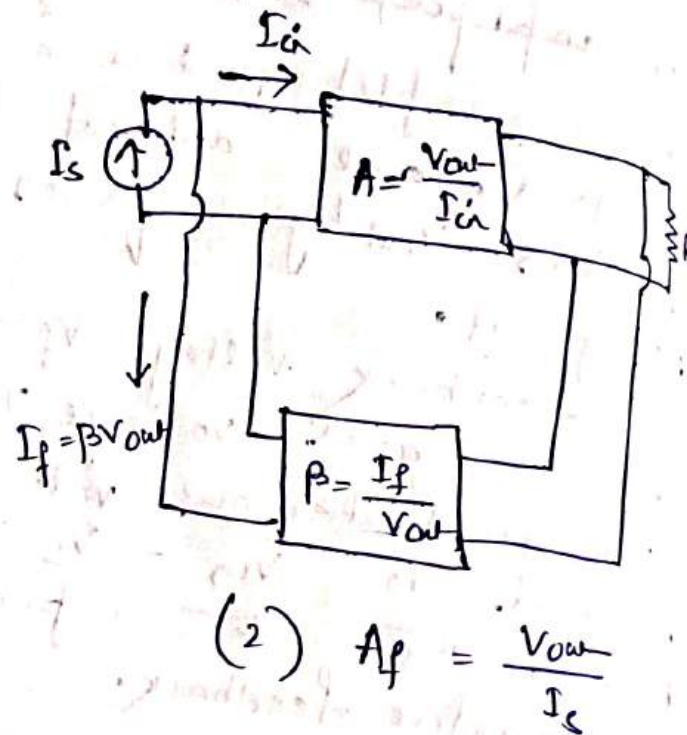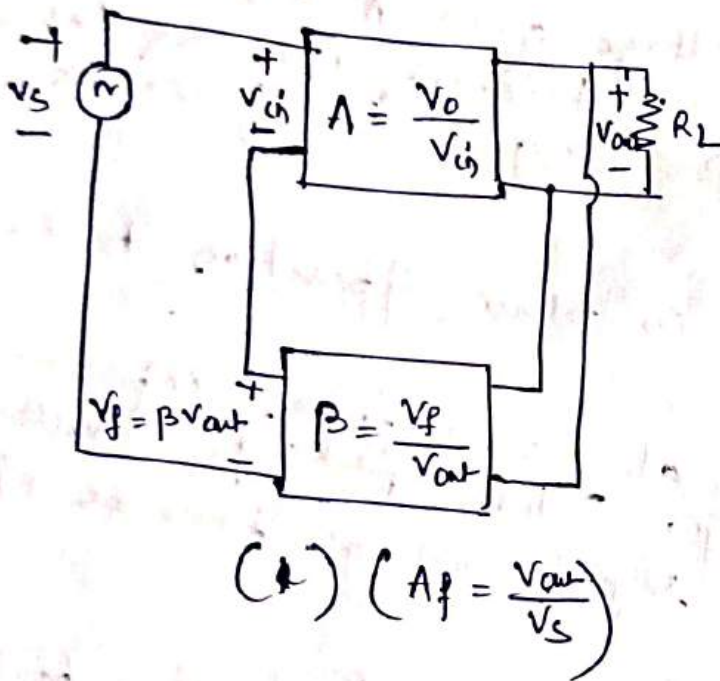1. Voltage - series feedback
2. Voltage - shunt feedback
3. Current - series feedback
4. Current - shunt feedback




→ Series refers to connecting the feedback signal in series with the input signal voltage.

Shunt refers to connecting the feedback signal in shunt with an input current source.

→ Series feedback connections tend to increase the input resistance, whereas shunt feedback connections tend to decrease the input resistance.

→ Voltage feedback tends to decrease the output impedance, whereas current feedback tends to increase the output impedance.

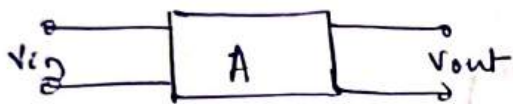
### Principle of Feedback in Amplifiers :-



For an ordinary amplifier, the voltage gain equals the ratio of output voltage and input voltage as

$$\text{Voltage gain } A = \frac{V_{out}}{V_{in}}$$

The gain is called the open-loop gain.

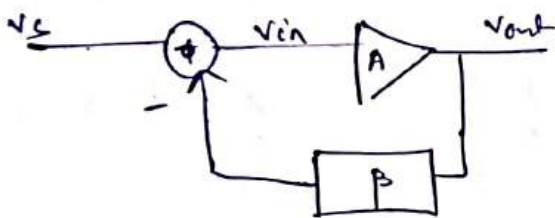

In this figure, let a fraction ( $\beta$ ) of the output voltage  $V_{out}$  will be supplied back to the input and  $A$

be the open-loop gain.

Now, the input voltage becomes

$$V_{in} = V_s + V_f = V_s + \beta V_{out} \quad (\text{Positive feedback})$$

$$V_{in} = V_s - V_f = V_s - \beta V_{out} \quad (\text{Negative feedback})$$

$$\boxed{V_{in} = V_s \pm \beta \cdot V_{out}}$$

### Negative feedback :-

Actual input voltage to amplifier  $V_{in} = V_s - \beta V_{out}$

The output voltage  $V_{out}$  must be equal to the input voltage  $(V_s - \beta V_{out})$  multiplied by the amplifier gain  $A$ .

$$V_{out} = A (V_s - \beta V_{out})$$

$$(1 + A\beta) V_{out} = A V_s$$

$$\Rightarrow \boxed{\frac{V_{out}}{V_s} = \frac{A}{1 + A\beta}} \quad A_f = \frac{V_{out}}{V_s} = \text{closed-loop gain}$$

### Positive feedback

Actual input voltage to amplifier

$$V_{in} = V_s + \beta V_{out}$$

The output voltage is given by

$$V_{out} = A (V_s + \beta V_{out})$$

$$\Rightarrow (1 - A\beta) V_{out} = A V_s$$

$$\Rightarrow \boxed{A_f = \frac{V_{out}}{V_s} = \frac{A}{1 - A\beta}}$$

$PA =$  feedback factor

$\beta =$  feedback ratio

\* If  $(1 - \beta A) < 1$ ,  $A_f$  exceeds  $A$ .  
Positive feedback increases the gain, but it reduces the stability and increases the distortion.

\* If  $(1 - \beta A) = 0$ ,  $A_f = \infty$ .

Thus, the amplifier is capable of giving output voltage even with zero signal.

\*  $(1 - \beta A) > 1$ ,  $A_f < A$ .

This happens in negative feedback.

Q Voltage gain of an amplifier without feedback is 60 db. It decreases to 40 db with feedback. Calculate the feedback factor.

Q A single stage transistor amplifier has a voltage gain of 600 without feedback, and 50 with feedback. Calculate the % age of output which is feedback to the input.

Q An amplifier with a negative feedback provides an output voltage of 5V with an input voltage of 0.2V. On removal of feedback, it needs only 0.1V input to give the same output. Determine (i) gain without feedback (ii) gain with feedback (iii) feedback ratio.

Q A negative feedback of  $\beta = 0.002$  is applied to an amplifier of gain 1000. Calculate the change in overall gain of the feedback amplifier if the internal amplifier is subjected to a gain reduction of 15%.

Advantages of Negative feedback

There are numerous advantages of negative feedback.

a. Gain stability :-  $A_f = A / (1 + A\beta)$ . If  $A\beta \gg 1$   
 $A_f \approx \frac{1}{\beta}$  i.e. overall gain of feedback amplifier ( $A_f$ ) depends on  $\beta$  which depends on the passive elements such as resistors. Resistors remain fairly constant and so the gain is stabilised.

b. Reduced Non-linear distortion :- The non-linear distortion is reduced by a factor  $(1 + A\beta)$  when negative feedback is used.

(Viva)

c. Reduced Noise:- There is always a noise voltage in the amplifier which is reduced by a factor  $(1+AP)$  when negative feedback is used.

d. Increased Bandwidth (Improved frequency response):-  
The bandwidth (BW) of an amplifier without feedback is equal to the separation between 3 dB frequencies  $f_1$  and  $f_2$ .

If  $A$  is the gain then gain-bandwidth product is  $A \times BW$ .  
With the negative feedback the amplifier gain is reduced and since gain-bandwidth product has to remain constant, the bandwidth will increase to compensate for the reduction in gain.

e. Increased Input Impedance:- The input impedance of the amplifier is increased by a factor  $(1+AP)$ .

f. Reduced output impedance:- The output impedance is reduced by a factor  $(1+AP)$ .

### Voltage-Series feedback:-

Voltage-series feedback refers to the connection connecting a part of the output voltage fed back in series with the input signal, resulting in an overall gain reduction.

With no feedback,  $A = \frac{V_o}{V_s} = \frac{V_o}{V_{in}}$

$$A = \frac{V_o}{V_s} = \frac{V_o}{V_{in}}$$

If a feedback signal  $V_f$  is connected in series with the input, then

$$V_{in} = V_s - V_f$$