

SUBJECT-BASIC ELECTRONICS ENGINEERING

TOPIC-OPERATIONAL AMPLIFIER

Name of the faculty-Mr. Bikash Meher

Assistant Professor

Department-EE

OPERATIONAL AMPLIFIER

Operational Amplifier (OP-Amp)

An operational amplifier is a very high gain amplifier having very high input impedance (in $M\Omega$ or more) and low output impedance (less than 100Ω).

The operational amplifier amplifies the signal and also performs the mathematical operations like addition, subtraction, integration etc., that's why it is named as op-amp.

One basic op-amp circuit is shown in fig 1.

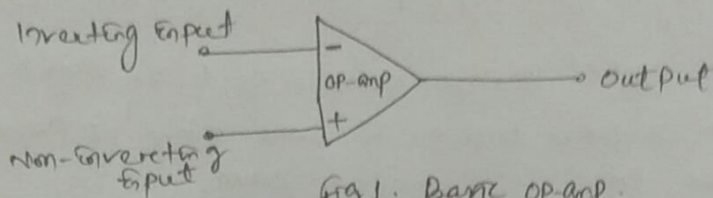


Fig 1. Basic op-amp.

It has two inputs: (i) Inverting (ii) Non-Inverting.

→ The (+) input produces an output that is in phase with the input signal applied, whereas the (-) input to the terminal results in an opposite-polarity output.

Ideal characteristics of op-amp :-

- 1) Voltage gain (A_v) is infinite.
- 2) Input impedance is infinite.
- 3) Input offset voltage is zero.
- 4) Output voltage range is infinite.
- 5) Bandwidth is infinite.
- 6) Slew rate is infinite.
- 7) Output impedance is zero.
- 8) Common mode rejection ratio (CMRR) is infinite.

BASIC OP-AMP.

The basic ckt connection using op-amp is shown in fig 2.


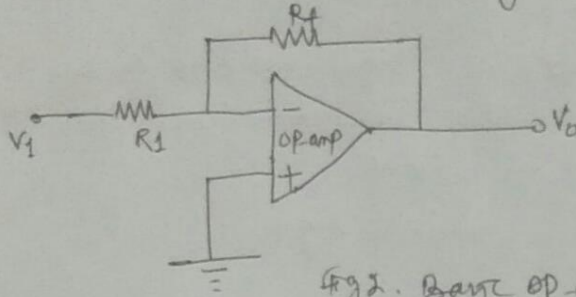



fig 2. Basic op-amp connection

An inp signal V_1 is applied through resistor R_1 to the inverting inp. The op is then connected back to the same inverting inp through resistor R_f . The plus input is connected ground.

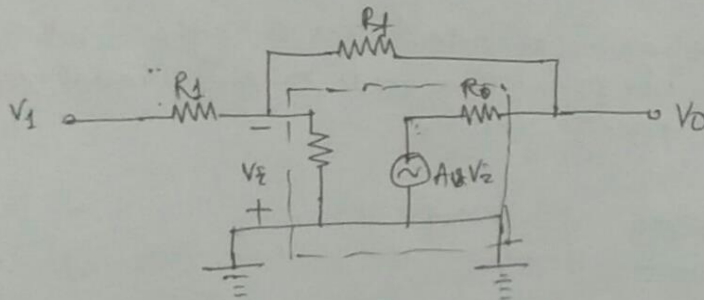
Now draw the ^{ac} equivalent ckt. (ideal condition)



(a)

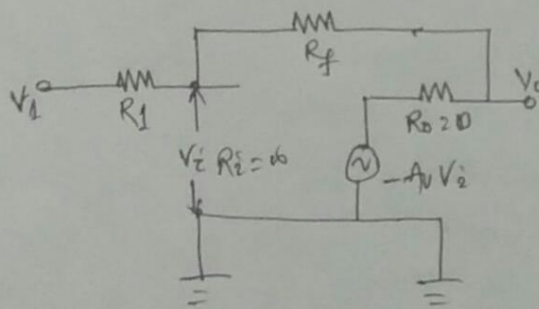

(b)

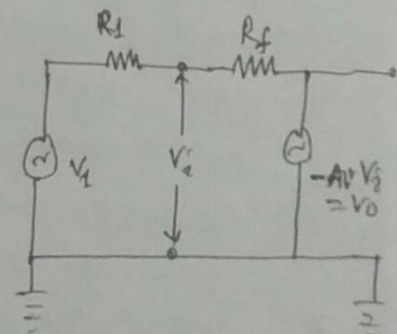

(c)

fig(a). operation of op-amp as constant gain multiplier.

- (a) op-amp ac equivalent ckt,
- (b) ideal op-amp eqⁿ ckt
- (c) retrans ckt.

2.

Here, we consider the ideal op-amp equivalent ckt., hence we replace $R_i = \infty$, $z_o = 0 \Omega$.

The ckt is redrawn as shown in fig 2c.

using superposition, we can solve for the voltage V_2 in terms of the components due to each of the sources.

For the source V_1 set ~~$V_2 = 0$~~ $-A_0 V_2 = 0$,

$$V_{21} = \frac{R_f}{R_1 + R_f} V_1$$

For the source $-A_0 V_2$; set $V_1 = 0$,

$$V_{22} = \frac{R_1}{R_1 + R_f} (-A_0 V_2)$$

The total voltage V_2 is then

$$V_2 = V_{21} + V_{22} = \frac{R_f}{R_1 + R_f} V_1 + \frac{R_1}{R_1 + R_f} (-A_0 V_2)$$

$$V_2 = \frac{R_f}{R_f + (1 + A_0)R_1} V_1$$

If $A_0 \gg 1$ and $A_0 R_1 \gg R_f$, then

$$V_2 = \frac{R_f}{A_0 R_1} V_1$$

Solving for V_0/V_2 , we get

$$\frac{V_0}{V_2} = \frac{-A_0 V_2}{V_2} = \frac{-A_0 R_f V_1}{V_2 A_0 R_1} = \frac{-R_f}{R_1} \frac{V_1}{V_2}$$

So that

$$\boxed{\frac{V_0}{V_1} = -\frac{R_f}{R_1}}$$

$$\boxed{A_V = -R_f/R_1}$$


Unity gain

If $R_f = R_1$, then the voltage gain

$$\text{voltage gain} = -R_f/R_1 = -1$$

Virtual ground :-

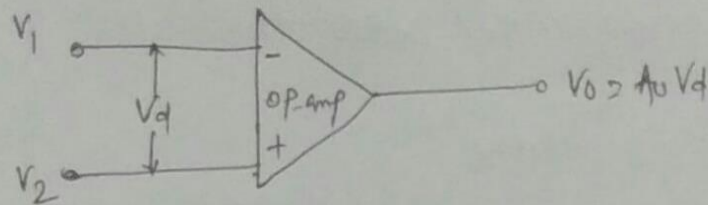In ideal condition, if one input is at zero potential, then the other terminal is also considered as at zero potential.



$V_1, V_2 \rightarrow$ Input voltages

$V_d \rightarrow$ difference voltage

$V_d = V_1 - V_2$, $A_o \rightarrow$ voltage gain

The diff voltage $(V_o) = A_o V_d$

$$\text{Now } A_o = \frac{V_o}{V_d}$$

$$= \frac{V_o}{V_1 - V_2}$$

We know that the voltage gain of the ideal op-amp is ∞ .

$$\text{So, } \infty = \frac{V_o}{V_1 - V_2} = \frac{V_o}{0V}$$

$$\therefore \Rightarrow V_1 - V_2 = 0V$$

$$\text{and } \boxed{V_1 = V_2}$$

Inverting Amplifier

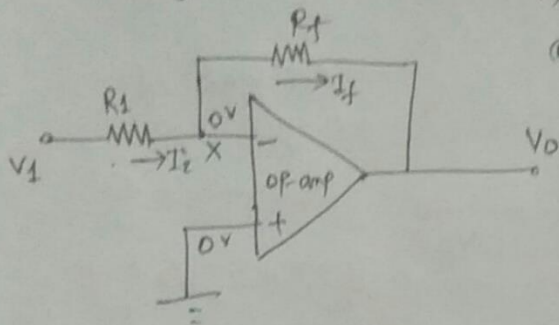


fig. Inverting op-amp configuration

In inverting amplifier, the input signal is applied to the (-) terminal. And the (+) terminal is connected to ground.

I_i is the inp current & I_f is feedback current.

Applying KCL at Node X.

As it's virtual ground concept the voltage at X is zero.

$$I_i = I_f$$

$$\frac{V_1 - 0V}{R_1} = \frac{0V - V_0}{R_f}$$

$$\Rightarrow \frac{V_1}{R_1} = -\frac{V_0}{R_f}$$

$$\Rightarrow \boxed{\frac{V_0}{V_1} = -R_f/R_1}$$

Non Inverting Amplifier :-

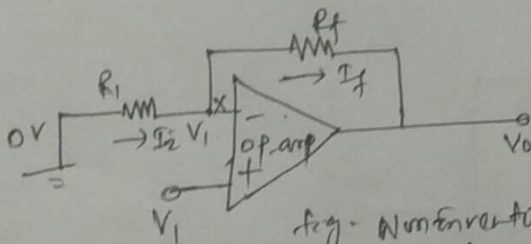


fig. Non Inverting Amplifier

In non-inverting amplifier, the input signal is applied to (+) terminal and (-) terminal is connected to ground.

Applying KCL at X, we get.

$$I_i = I_f$$

$$\Rightarrow \frac{0V - V_1}{R_1} = \frac{V_1 - V_0}{R_f}$$

$$\Rightarrow \frac{-V_1}{R_1} = \frac{V_1 - V_0}{R_f}$$

$$\Rightarrow \boxed{\frac{V_0}{V_1} = 1 + \frac{R_f}{R_1}}$$

Summing Amplifier :- It produces the sum of the input signals.

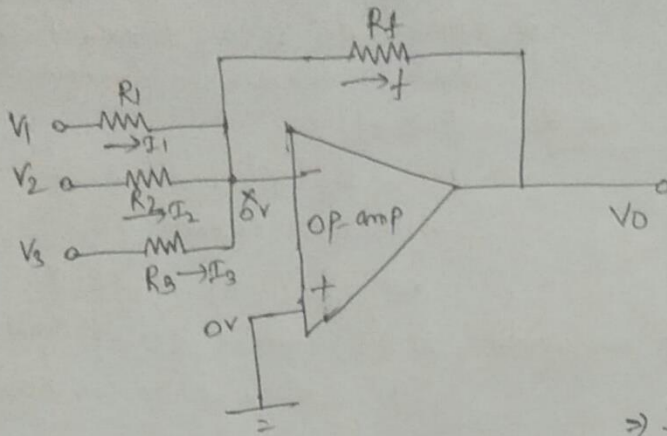


Fig. Summing amplifier

Applying KCL at X,
we get

$$I_1 + I_2 + I_3 = I_f$$

$$\Rightarrow \frac{V_1 - 0V}{R_1} + \frac{V_2 - 0V}{R_2} + \frac{V_3 - 0V}{R_3} = \frac{0V - V_0}{R_f}$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_0}{R_f}$$

$$\Rightarrow V_0 = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

If $R_f = R_1 = R_2 = R_3$

$$V_0 = -(V_1 + V_2 + V_3)$$

The op of the summing amplifier is the summation of all the input signals.

Subtractor ~~is~~ is Differential amplifier :-

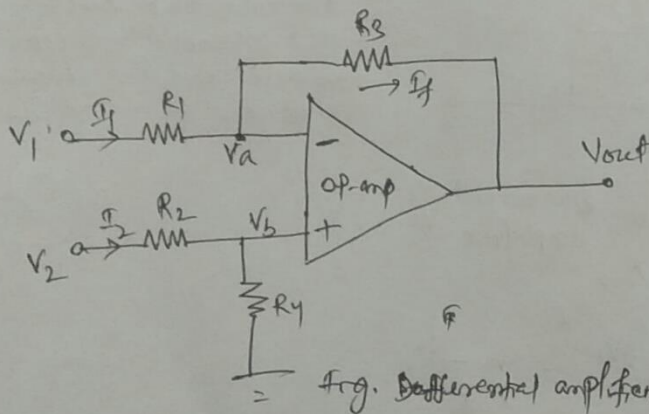


Fig. Differential amplifier

From the fig. we can find

$$I_1 = \frac{V_1 - V_a}{R_1},$$

$$I_2 = \frac{V_2 - V_b}{R_2},$$

$$I_3 = \frac{V_a - V_{out}}{R_3}$$

As per the virtual ground concept, $V_a = V_b$.

and $V_b = V_2 \left(\frac{R_4}{R_2 + R_4} \right)$

If $V_2 = 0$; then; $V_{out(a)} = -V_1 \left(\frac{R_3}{R_1} \right)$

If $V_1 = 0$; then,

$$V_{out(b)} = V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(1 + \frac{R_3}{R_1} \right)$$

↑
Using voltage division


$$V_{out} = -V_{out(a)} + V_{out(b)}$$

$$\therefore V_{out} = -V_1 \left(\frac{R_3}{R_1} \right) + V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(1 + \frac{R_3}{R_1} \right)$$

If $R_1 = R_2 = R_3 = R_4$, then we

$$\boxed{V_{out} = V_2 - V_1}$$

Integrator circuit

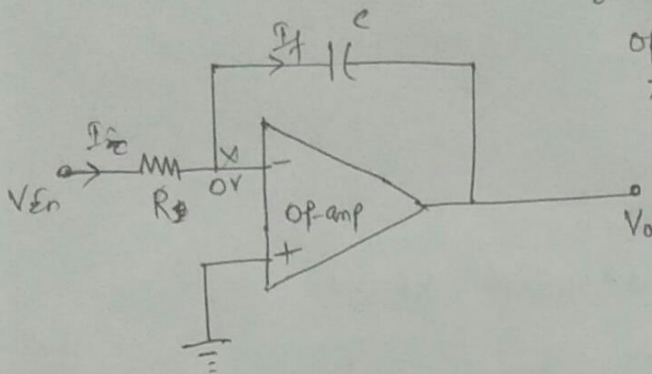

The op-amp integrator is an operational amplifier circuit that performs the mathematical operation of integration.

→ The integrator produces an output voltage which is proportional to the integral of the input voltage.

Fig. Integrator ckt

Applying KCL at X, we get


$$I_i = I_f$$

$$\Rightarrow \frac{V_{in} - 0V}{R_1} = C \frac{d(V_{in} - V_o)}{dt}$$

$$\Rightarrow \frac{V_{in}}{R_1} = -C \frac{dV_o}{dt}$$

$$\Rightarrow \boxed{V_o = -\frac{1}{RC} \int V_{in} dt}$$

Differentiator amplifier

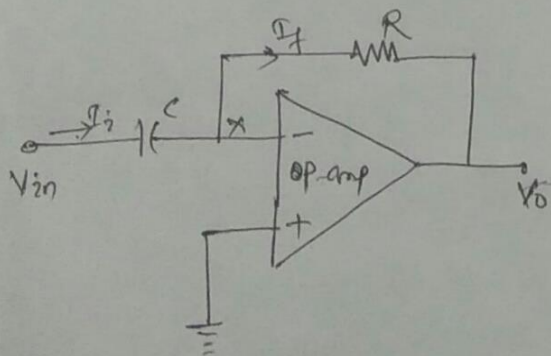

The op-amp differentiator is an operational amplifier circuit that performs the mathematical operation of differentiation.

The differentiator produces an output voltage which is directly proportional to the input voltage's rate-of-change with respect to time.

Applying KCL at X, we get

$$I_{in} = I_f$$

$$\Rightarrow \frac{C d(V_{in} - 0V)}{dt} = \frac{0V - V_o}{R}$$


$$\Rightarrow \frac{C dV_{in}}{dt} = -\frac{V_o}{R}$$

$$\Rightarrow \boxed{V_o = -RC \frac{dV_{in}}{dt}}$$

CMRR (Common mode rejection ratio)

The CMRR is defined as, it is the ratio between differential gain (A_d) to common mode gain (A_c).

$$CMRR = \frac{A_d}{A_c}$$

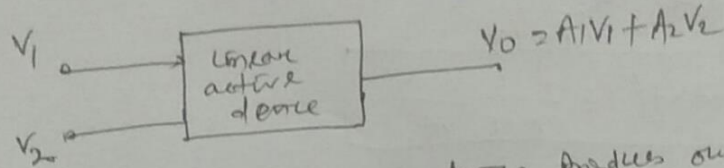

Let us consider a linear active device produces output V_0 is the linear combination of inputs.

The difference voltage is defined as

$$V_d = V_1 - V_2 \quad \text{--- (1)}$$

and the common mode voltage is defined as

$$V_c = \frac{V_1 + V_2}{2} \quad \text{--- (2)}$$

Subtract eqn (2) from eqn (1)

$$\begin{array}{r} V_d = V_1 - V_2 \\ 2V_c = V_1 + V_2 \\ \hline V_d - 2V_c = -2V_2 \end{array}$$

$$\Rightarrow V_2 = \frac{V_d - 2V_c}{-2}$$

Add eqn (1) with eqn (2)

$$\begin{array}{r} V_d = V_1 - V_2 \\ 2V_c = V_1 + V_2 \\ \hline V_d + 2V_c = 2V_1 \end{array}$$

$$\Rightarrow V_1 = V_c + \frac{V_d}{2}$$

Substitute the value of V_1 and V_2 in $V_0 = A_1V_1 + A_2V_2$.

$$\begin{aligned} \text{So, } V_0 &= A_1 \left(V_c + \frac{V_d}{2} \right) + A_2 \left(V_c - \frac{V_d}{2} \right) \\ &= A_1 V_c + \frac{A_1 V_d}{2} + A_2 V_c - \frac{A_2 V_d}{2} \\ &= (A_1 + A_2) V_c + \frac{(A_1 - A_2)}{2} V_d \end{aligned}$$

$$V_0 = A_c V_c + A_d V_d$$

where $A_1 + A_2 = A_c$
 $\& \frac{A_1 - A_2}{2} = A_d$

$A_c \rightarrow$ common mode gain of the amplifier
 $A_d \rightarrow$ differential gain of the amplifier.

$$\text{CMRR in dB} = 20 \log_{10} \frac{A_d}{A_c}$$

$$V_o = A_d V_d + A_c V_c$$

$$= A_d V_d \left(1 + \frac{A_c V_c}{A_d V_d} \right)$$

$$V_o = A_d V_d \left(1 + \frac{1}{\text{CMRR}} \frac{V_c}{V_d} \right)$$